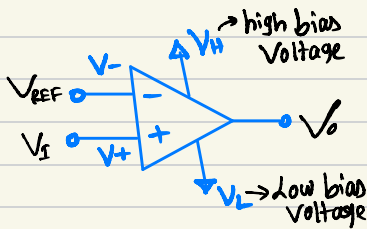


Schmitt Trigger Circuit



Otto H. Schmitt (1934) → an electrical engineer proposed this ckt.

Comparators


① Non-Inverting Comparator



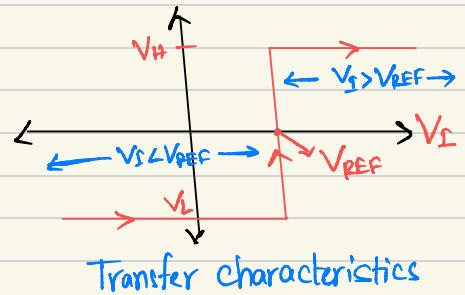
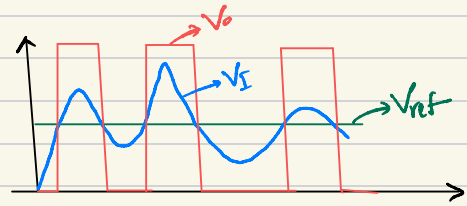
$$\begin{aligned} \rightarrow V_I > V_{REF} &\rightarrow V_O = V_H \\ \rightarrow V_I < V_{REF} &\rightarrow V_O = V_L \end{aligned}$$



② Inverting Comparator


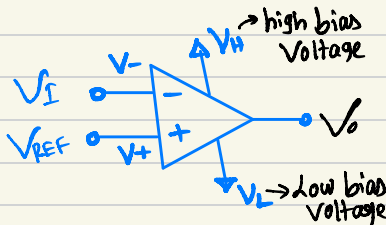

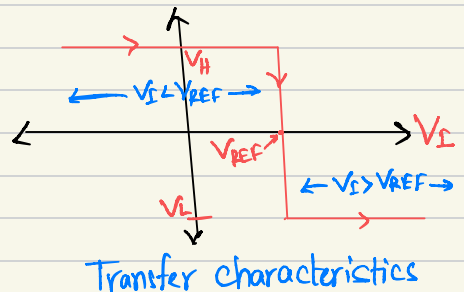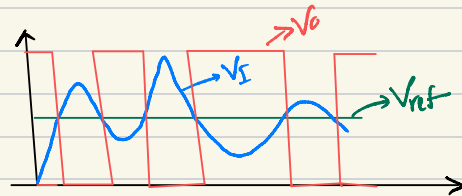
$$\begin{aligned} \rightarrow V_I > V_{REF} &\rightarrow V_O = V_L \\ \rightarrow V_I < V_{REF} &\rightarrow V_O = V_H \end{aligned}$$




③ Non-Inverting comparator with ref. voltage:

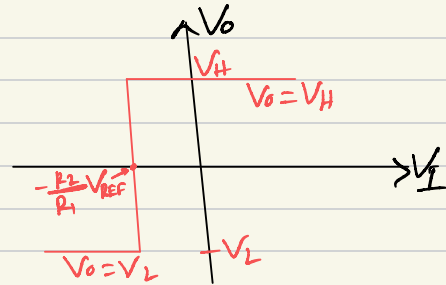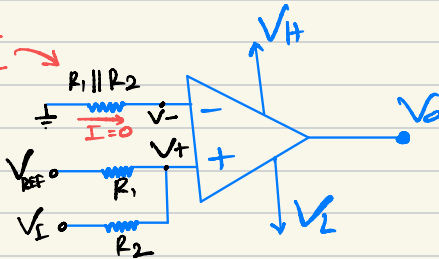This prevent DC bias effect inside op-amp



$\rightarrow I=0 \rightarrow V-=0$ always

Node equation at $V+$

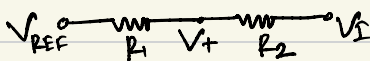

$$\frac{V+ - V_{REF}}{R_1} + \frac{V+ - V_I}{R_2} = 0$$

$$\begin{cases} V+ = V_{REF} \left(\frac{R_2}{R_1 + R_2} \right) + V_I \left(\frac{R_1}{R_1 + R_2} \right) \\ V- = 0 \end{cases}$$

Now,
 $V+ > V- \rightarrow V_0 = V_H$

$$\Rightarrow \frac{V_I R_1}{R_1 + R_2} + \frac{V_{REF} R_2}{R_1 + R_2} > 0$$



$$\therefore V_I > \left(-\frac{R_2}{R_1} \right) V_{REF}$$

$$\boxed{V_0 = V_H}$$

and $V_I < \left(-\frac{R_2}{R_1} \right) V_{REF}$

$$\boxed{V_0 = V_L}$$

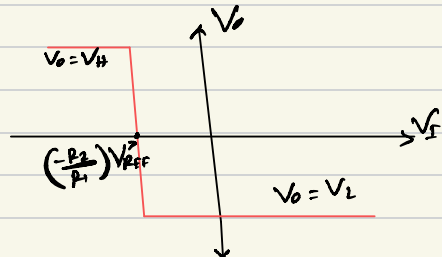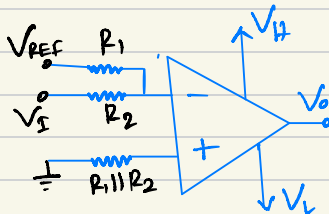④ Inverting comparator with ref. voltage:



$$V+ = 0$$

$$V- = V_I \frac{R_1}{R_1 + R_2} + V_{REF} \frac{R_2}{R_1 + R_2}$$

$$\rightarrow \text{if } V_I < \left(-\frac{R_2}{R_1} \right) V_{REF} \rightarrow V_0 = V_H$$

$$\rightarrow \text{if } V_I > \left(-\frac{R_2}{R_1} \right) V_{REF} \rightarrow V_0 = V_L$$