



# BRAC UNIVERSITY

CSE 350: Digital Electronics and Pulse techniques

Exp-01: Implementing Diode Logic (DL) gates

---

## Objectives

1. Construct Diode Logic (DL) gates.
2. Understanding the circuit operations.

## Equipment and component list

### *Equipment*

1. Digital Multimeter
2. DC power supply

### *Component*

- NPN Transistor (C828) - x1 piece
- Diode 1N4003 - x2 pieces
- Resistors -
  - ◆ 450  $\Omega$  - x2 piece
  - ◆ 15 K $\Omega$  - x1 piece
  - ◆ 2.2 K $\Omega$  - x1 piece
  - ◆ 100 K $\Omega$  - x1 piece

 


Fig 1: OR gate

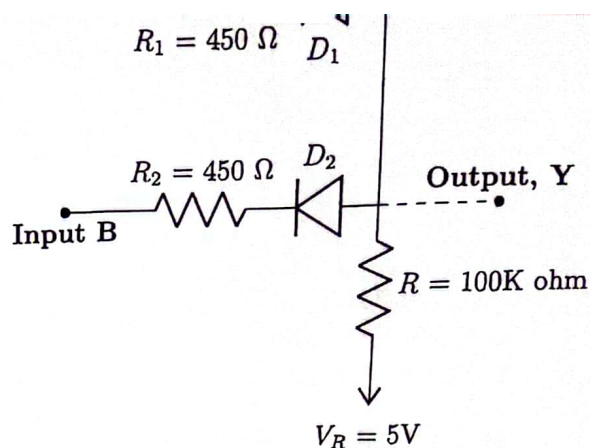


Fig 2: AND gate

## Task-01: OR gate

### THEORY

In digital logic, a 2-input OR gate outputs a logical HIGH if at least one of the inputs is HIGH. Otherwise, the output of the OR gate is logical LOW.

In this task, we will implement a Diode Logic (DL) OR gate. In Fig. 1, we can see two input nodes (A and B) and one output node (Y) of the OR gate. We will consider 5V as logical HIGH input and 0V as logical LOW input in our experiment. Now, if any of the inputs are set to 5V, the corresponding diode is turned on. As a result, a current flows through that diode. This current ultimately flows through  $R$  towards the ground, thus creating a voltage drop across the  $R$  resistor. As  $R_1$  and  $R_2$  resistors are very small compared to  $R$ , the voltage drop across  $R$  will be close to 5V. In this case, we will consider the obtained output voltage at node Y to be logically HIGH. Next, if all the inputs are set to 0V, no current flows through the diodes and resistor  $R$ . As a result, the voltage drop across  $R$  will be zero. So, the output voltage will be 0V, which we will consider to be logically LOW.

## Task-02: AND gate

### THEORY

In digital logic, a 2-input AND gate outputs a logical LOW if at least one of the inputs is LOW. Otherwise, the output of the AND gate is logical HIGH.

Similar to the previous task, we will implement a Diode Logic (DL) AND gate. If any of the inputs are set to 0V, the corresponding diode is turned on. As a result, a current flows through that diode from the  $V_R$  voltage source. This current flows through  $R$  and creates a voltage drop across the resistor. As  $R_1$  and  $R_2$  resistors are very small compared to  $R$ , the voltage drop across  $R$  will be close to 5V. As a result, the obtained output voltage at node Y will be close to 0V which we will consider as logically LOW. Next, if all the inputs are set to 5V, no current flows through the diodes and resistor  $R$ . Therefore, the voltage drop across  $R$  will be zero. So, the output voltage will be the same as  $V_R$  or 5V, which is logically HIGH.

## Task-03: Inverter (NOT gate)

### THEORY

In digital logic, an inverter or NOT gate is a logic gate which implements logical negation. It has a single input and a single output where the output is the exact opposite of the input. Meaning, if the input is Logical High, the output will be Logical Low and vice versa. The RTL implementation of an inverter circuit is shown in Figure 03.

Here the input is applied to the base of a Transistor or, BJT ( $Q_1$ ) through the resistor  $R_1$  and the output is available at the collector terminal (point Y). We connect the ground terminal to the emitter node directly and to the base node through the resistor  $R_2$ . Hence, when the input  $V_i$  is LOW (0V), the 'Base' terminal



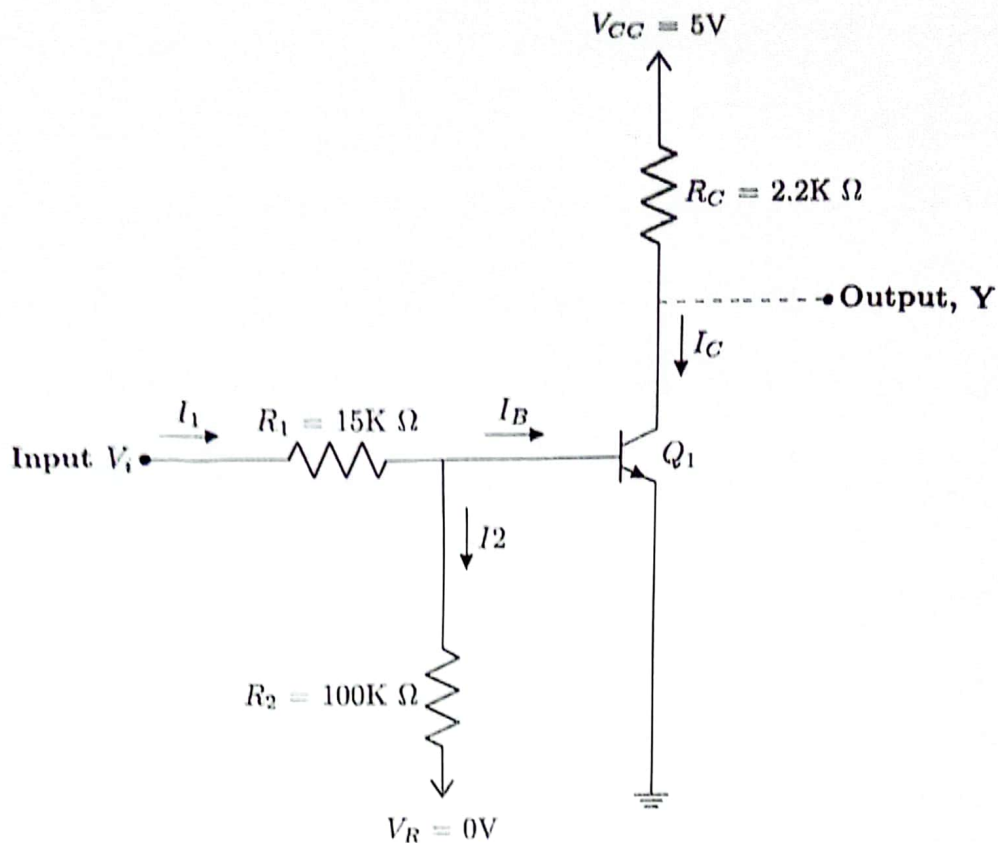


Fig 3: Inverter (NOT gate)

of the transistor cannot be at a voltage higher than zero. For  $Q_1$  to be turned ON, the Base-Emitter voltage difference must be greater than 0.5V. Thus, the BJT cannot turn ON when the input is LOW and operates in cutoff mode. This means  $Q_1$  acts like an open circuit and the current passing through the  $R_C$  resistor ( $I_C$ ) is zero. As a result, there will be no voltage drop in the resistor  $R_C$  and the voltage of the output point (Y) will be same as  $V_{CC} = 5V$  (High).

On the other hand, if a HIGH input (5V) is applied at the input terminal ( $V_i$ ),  $Q_1$  will be driven into saturation mode. In this mode, the Collector-Emitter voltage difference ( $V_{CE}$ ) is nearly 0.2V. As the emitter is connected to the ground terminal, the emitter voltage ( $V_E$ ) is zero. Hence, the collector voltage will be close to 0.2V (LOW). Thus, the output of the circuit is always the opposite of the input.

### Procedure:

1. Connect the circuit as shown in Fig: 1, 2 & 3.
2. Observe the output for all possible input combinations and thus verify the type of gate.
3. Fill up the following tables for OR gate, AND gate and Inverter.

## Data Tables

$V_A(V)$	$V_B(V)$	$V_{R1}(V)$	$V_{R2}(V)$	$I_{R1}(mA)$	$I_{R2}(mA)$	$V_Y(V)$
0	0	0	0	0	0	0
0	5	0	0.7	0	1.55	4.1
5	0	0.7	0	1.55	0	4.1
5	5	0.35	0.35	0.577	0.577	4.29

Table 1: Table for OR Gate

$V_A(V)$	$V_B(V)$	$V_{R1}(V)$	$V_{R2}(V)$	$I_{R1}(mA)$	$I_{R2}(mA)$	$V_Y(V)$
0	0	0.7	0.7	1.55	1.55	0
0	5	0.7	0	1.55	0	0.67
5	0	0	0.7	0	1.55	0.67
5	5	0	0	0	0	5

Table 2: Table for AND Gate

$V_i$ (V)	$V_{R1}$ (V)	$V_{R2}$ (V)	$V_{RC}$ (V)	$I_1$ (mA)	$I_2$ (mA)	$I_B$ (mA)	$I_C$ (mA)	$V_Y$ (V)
0	0	0	0	0	0	0	0	5
5	4.3	0	4.8	0.286	0.043	0.043	2.18	0.2

Table 3: Table for RTL inverter

## Report

Please answer the following questions briefly in the given space.

1. Verify that the transistor will be operating in the saturation and cutoff region in two cases for the inverter circuit (Use experimental data for verification).

Ans. From data at  $V_A$  and  $V_B = 0.0V$ ,  $I_B = I_C$  and  $I_E = I_B + I_C = 0$

so this is cutoff region. So in  $V_i = \text{Low}$  then transistor is in cutoff region. When  $V_i = 5.03V$  then  $I_B = 0.266mA$  and  $I_C = 2.31mA$ . We know at saturation region

$\frac{I_C}{I_B} < \beta$ , so, it is in saturation region.

2. For OR gate circuit, should  $I_{R_1}$  and  $I_{R_2}$  be equal theoretically when  $V_A = V_B = 5V$ ? Did you obtain a similar result in your experiment? Explain briefly.

Ans. At  $V_A = V_B = 5V$ , we got values for  $I_{R_1}, I_{R_2} = 0mA$

$R_1 = R_2$  which are connected across  $5V$  &  $0.7V$  voltage drop across resistor is same.

So, current will be same. But I didn't get similar results in experiment. It both has little different and not similar with if 1 voltage has changed with other voltage inputs.

3. (For both OR & AND gate circuits) Will the diodes  $D_1$  and  $D_2$  turn ON, if  $V_A = V_B = 6V$  and  $V_R = 5V$ ? Explain briefly.

Ans. For OR gate,

$$V_R = 5V; I_R = \frac{5-0}{100} = 0.05mA$$

$$V_A = V_B; I_{R_1} = I_{R_2} = 0.025mA$$

$$\therefore 0.025 = \frac{6-x}{0.450} \Rightarrow x = 5.99V$$

It is greater than  $5+0.7V$  so,

$D_1$  &  $D_2$  will be on.

For AND Gate,

$$x = 5.99 \neq 0.7$$

$\therefore D_1$  and  $D_2$  will be off.




4. What is the function of  $V_R = 0V$  at the base of an inverter in figure 3?

Ans.

$V_R = 0V$  means input voltage  $V_i$  is Low, the base-emitter voltage  $V_{BE}$  is insufficient to turn on the transistor. It is cutoff region.

5. Assuming OR gate, Draw the output.

 

Ans.

time	A	B	output
t <sub>1</sub>	1	1	1
t <sub>2</sub>	0	1	1
t <sub>3</sub>	0	0	0
t <sub>4</sub>	1	0	1
t <sub>5</sub>	0	1	1
t <sub>6</sub>	0	0	0
t <sub>7</sub>	1	0	1
t <sub>8</sub>	1	1	1

## Data Tables

$V_A(V)$	$V_B(V)$	$V_{R1}(V)$	$V_{R2}(V)$	$I_{R1}(mA)$	$I_{R2}(mA)$	$V_Y(V)$
0	0	0	0	0	0	0.07
0	5.03	0 ✓	677 mV	0	1.447	3.73
5.03	0	666 mV	0	1.442	0	3.72
5.03	5.03	368 mV	376.4 mV	0.796	0.814	4.06

Table 4: Table for OR Gate

$V_A(V)$	$V_B(V)$	$V_{R1}(V)$	$V_{R2}(V)$	$I_{R1}(mA)$	$I_{R2}(mA)$	$V_Y(V)$
0	0	5.7 mV	21.4 mV	0.012	0.045	0.419
0	5.03	21.5 mV	0.4 mV	0.465	0.008	0.4
5.03	0	0	21.4 mV	0	0.045	0.446
5.03	5.03	0	0.4 mV	0.011	0	4.97

Table 5: Table for AND Gate

$V_i$ (V)	$V_{R1}$ (V)	$V_{R2}$ (V)	$V_{Rc}$ (V)	$I_1$ (mA)	$I_2$ (mA)	$I_B$ (mA)	$I_C$ (mA)	$V_Y$ (V)
0	0	1.7 mV	2.1 mV	0	1.72	-1.72	0.976	5.02
5.03	4.08	0.68	4.97	0.272	0.006	0.266	2.31	34 mV

Table 6: Table for RTL inverter

Signature 6/6/24