
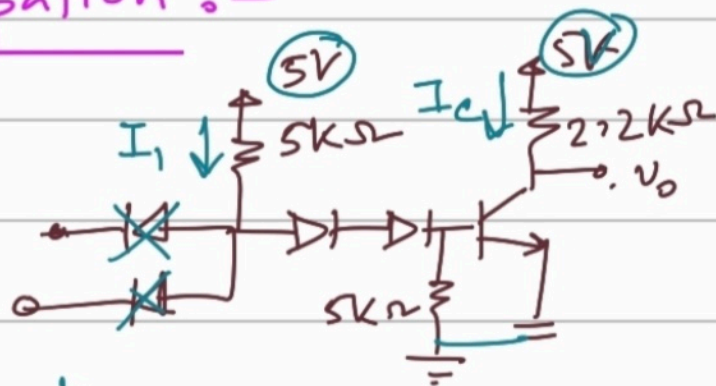



Maximum Power Dissipation :-

* Case ③ $V_A = V_B = 5V$

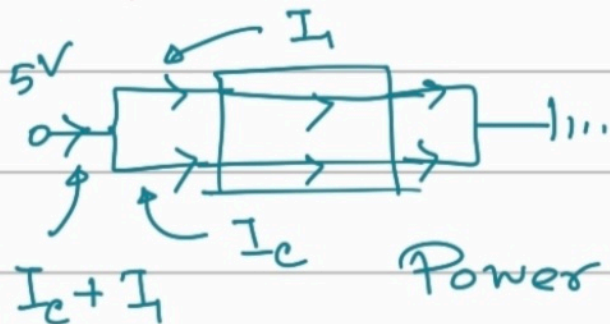

$$\begin{aligned} \text{Power dissipation} &= (5 - 0) \times (2.182 + 0.56) \\ &= \boxed{13.71 \text{ mW}} \end{aligned}$$


Case ① $V_A = V_B = 0.2$

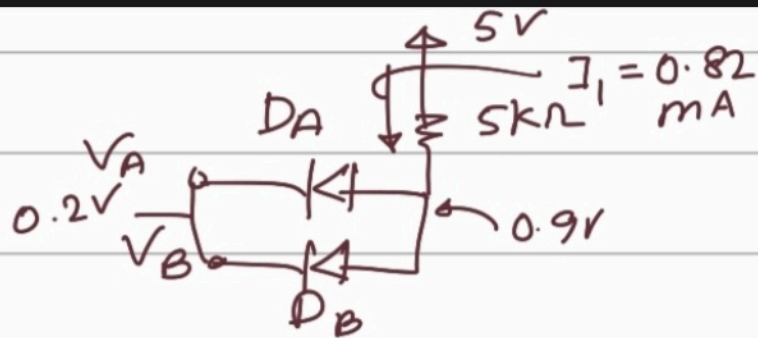

$$\begin{aligned} \text{Power dissipation, } &(5 - 0.2) \times 0.82 \\ &= \boxed{3.936 \text{ mW}} \end{aligned}$$


Maximum fanout Calculation :-

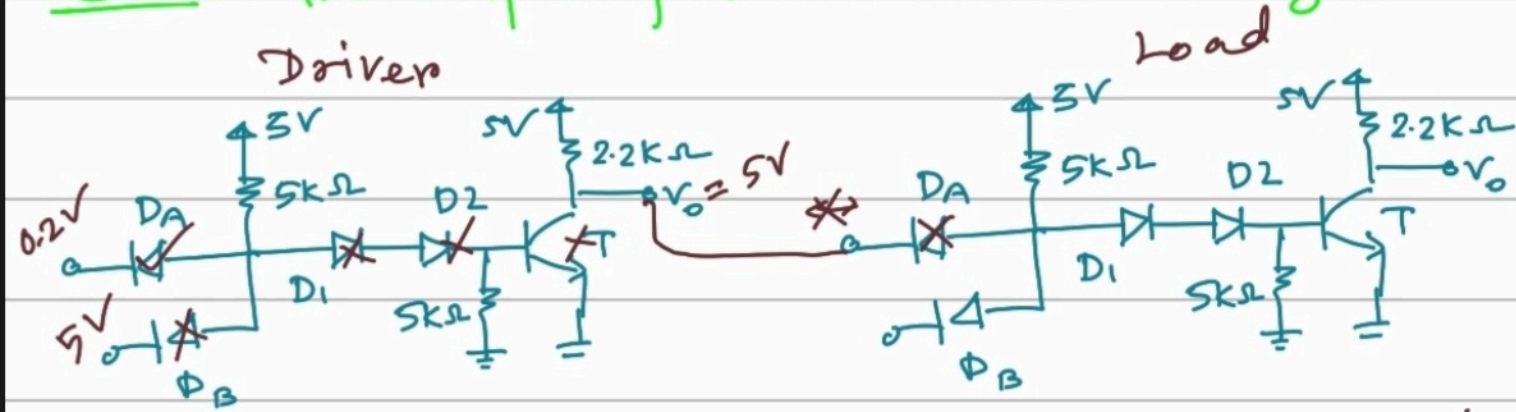Case ①. The output of driver circuit is high.



The demand current is zero, and supply is zero, also. Thus we can connect as much as load circuits we want. $\text{max Fanout} = \infty$.

Case ②. $V_o = 0.2V$

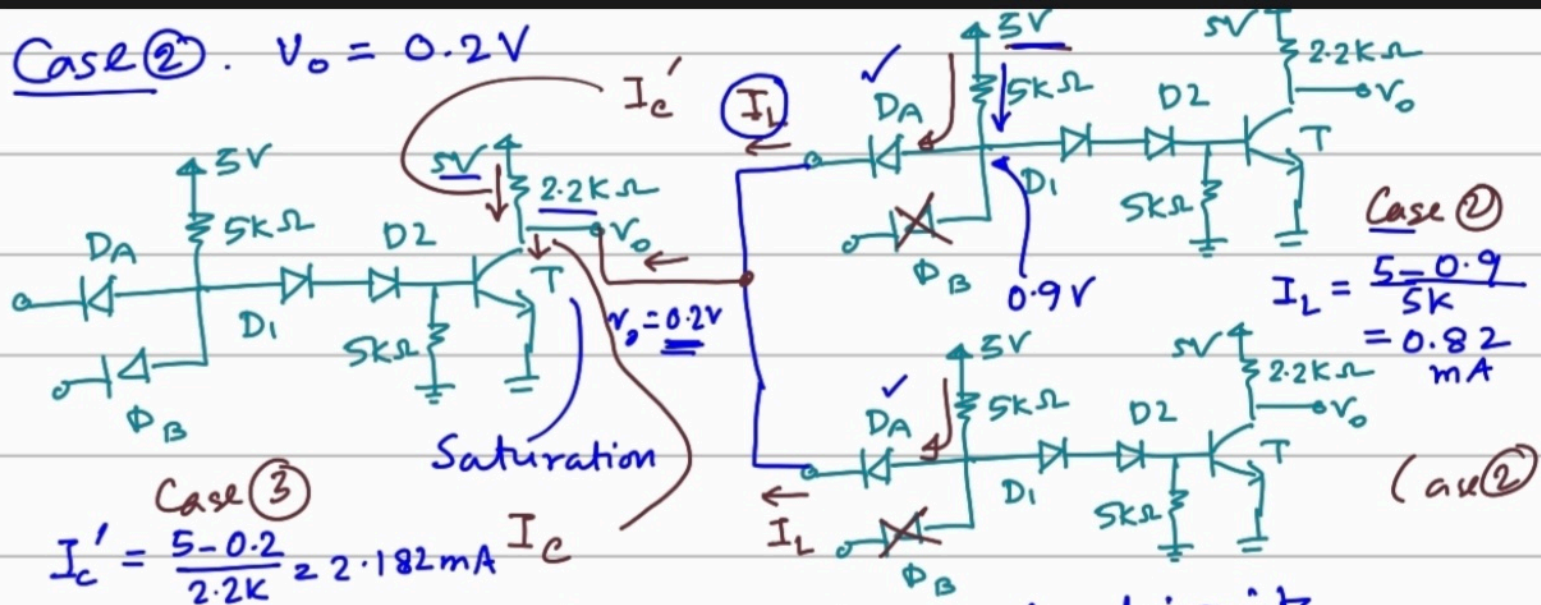

We want to consider worst case scenario, thus we will consider D_B of load circuits are off.

I_c = total collector current, I_c' = no. load collector current.
 I_L = standard load (current), N = fanout

$$I_c = I_c' + N I_L = 2.182 + N \times 0.82$$

transistor

Constraint: When driver circuit is operating in saturation mode, the collector current can not exceed a certain value. Otherwise, the driver transistor T will change its operating mode saturation to forward active.

Marginal situation will be achieved if

$\beta_{\text{forced}} \approx \beta_F$ for driver transistor T .

$$\beta_{\text{forced}} \approx \frac{I_c}{I_B} \Rightarrow I_{c,\text{max}} = \beta_F \times I_B = 30 \times 0.4 = 1.2 \text{ mA}$$

← Case ③

Maximum fanout is N' . Then the main equation becomes, $I_{c,\text{max}} = I_c' + N' I_L$

$$1.2 = 2.182 + N' \times 0.82$$

$$\Rightarrow N' = 11.96$$

We can not choose maximum fanout $N' = 12$

because that will exceed the value of permitted collector current.

Therefore, maximum fanout for this case $(N') = 11$

$$\text{Finally maximum fanout} = \min(11, \infty) = 11$$