


Node, KVL, KCL, Nodal Analysis

Charge: Fundamental property of elementary particles.

Atom $\leftarrow \{ \text{electron, proton, neutron} \}$

Coulomb's law is used to calculate the force between charged particle.

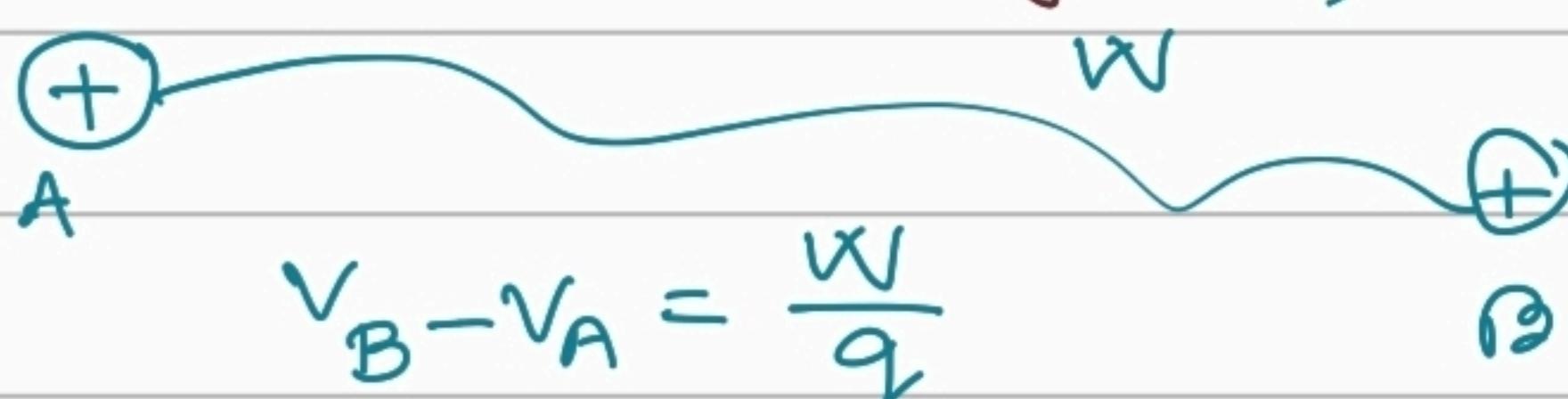Voltage: The amount of work $^{(1J)}$ needed to displace a $^{(1C)}$ unit charge from one point to another is called voltage. $(1V)$




Current: The rate of flow of charge within a conductor is called current.

$$\boxed{\frac{dq}{dt} = i}$$

SI unit of current is ampere.

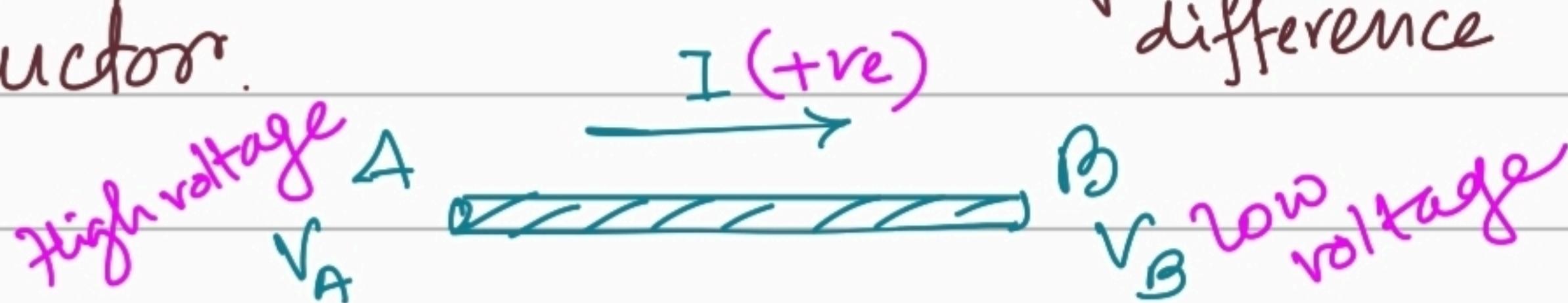Ohm's law: For a certain temperature the amount of current flows through a conductor is proportional to the voltage across the conductor.



$$I \propto (V_B - V_A) \Rightarrow I = G(V_B - V_A)$$

G → conductance

R → resistance

$$\begin{aligned} (V_B - V_A) &= RI = \frac{1}{G} I \\ V_{BA} &= RI \end{aligned}$$

Electrical Components

① Resistor:

$$R \neq 0$$

perfect conductor

$$R = 0$$

② Voltage Source:

$$V_s$$

internal resistance

$$V_1$$

Practical case

source resistance

V_1 doesn't depend on current.

③ Capacitor:


$$C \parallel V$$

parallel plate capacitor

The amount of charge stored in a capacitor is proportional to the voltage difference across the capacitor.

$$Q \propto V \Rightarrow Q = CV \quad | C \rightarrow \text{capacitance}$$

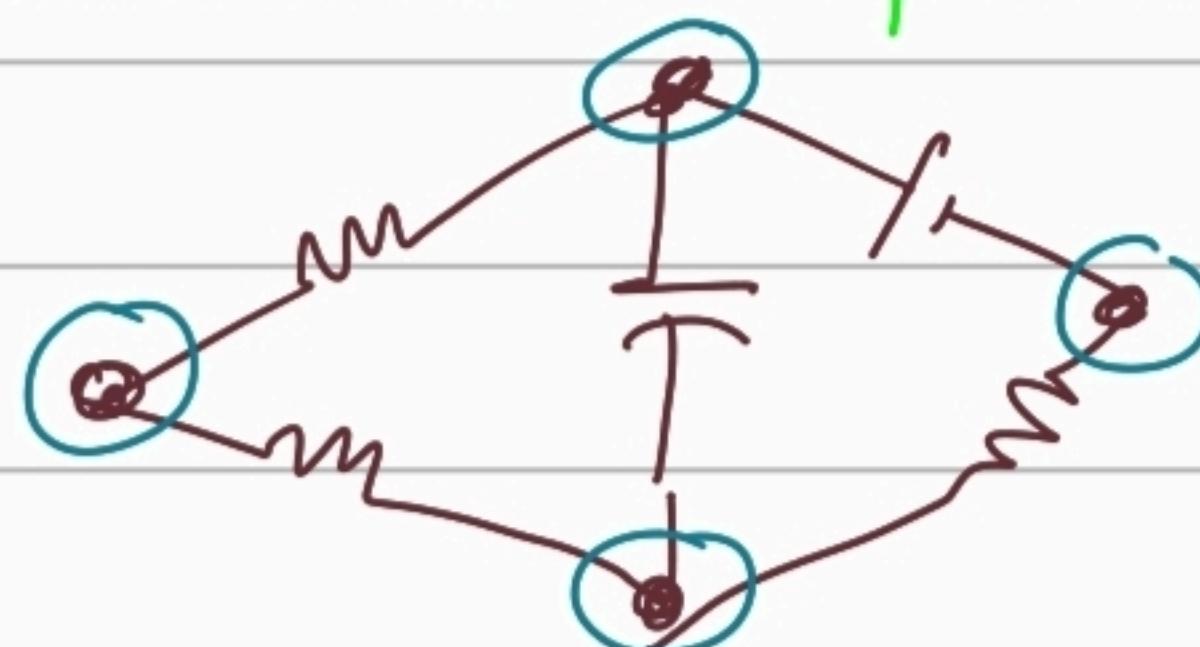Node: The interconnection point between more than one electrical component is called a node.




4 nodes

KCL : Kirchhoff's Current Law

The algebraic sum of currents on a node is zero.


$$-i_1 + i_2 + i_3 - i_4 + i_5 = 0$$

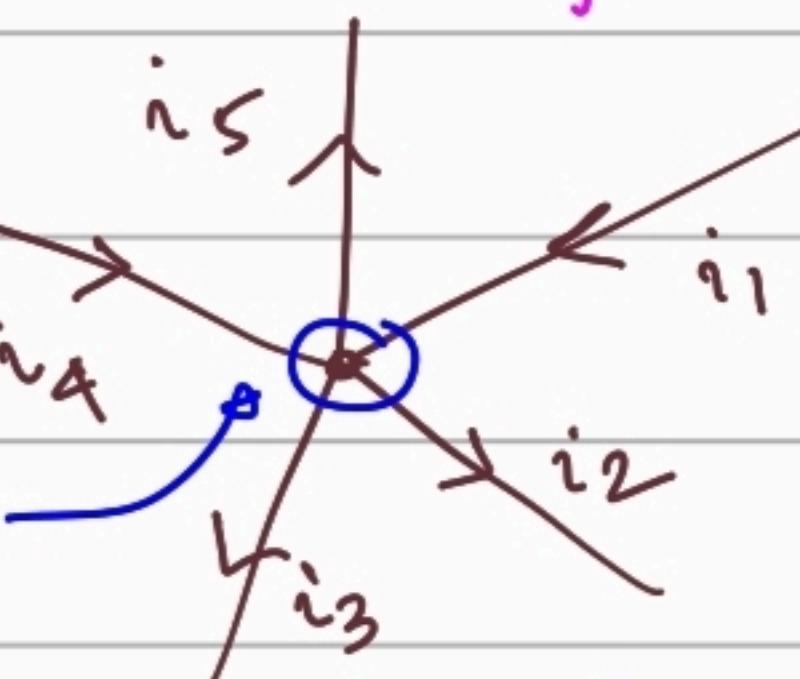

• current entering a node would be negative current

• current exiting a node would be positive current.

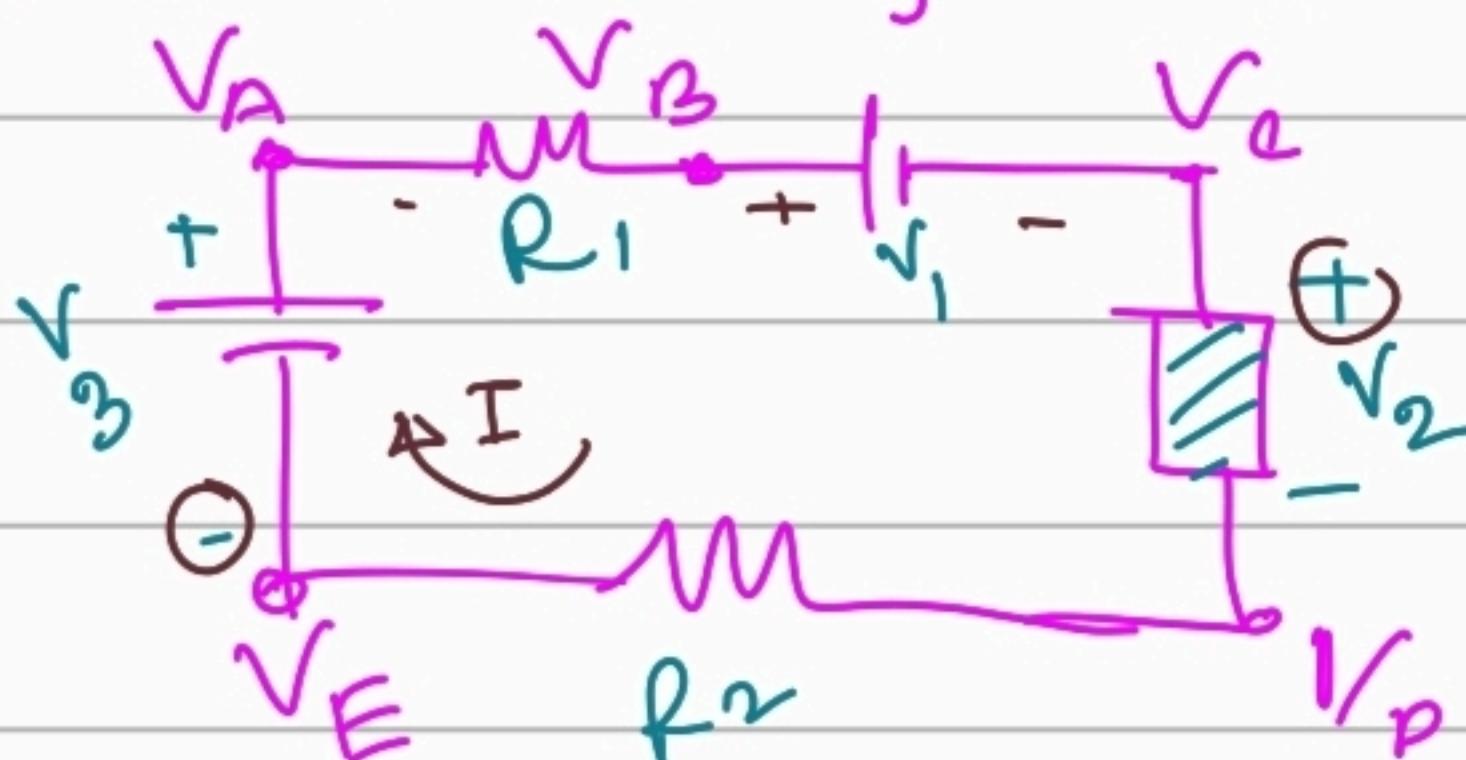KVL : The voltage drop across a loop inside a electric circuit is zero.




$$\underline{V_{AB} + V_{BC} + V_{CD}} + V_{DE} + V_{FA} = 0$$

$$IR_1 + V_1 + V_2 + IR_2 - V_3 = 0$$

NODE ANALYSIS :

1. Identify a reference node (ground)
2. Identify all the unknown node
3. Write the nodal equation
4. Solve the nodal equations together.

Example 1:

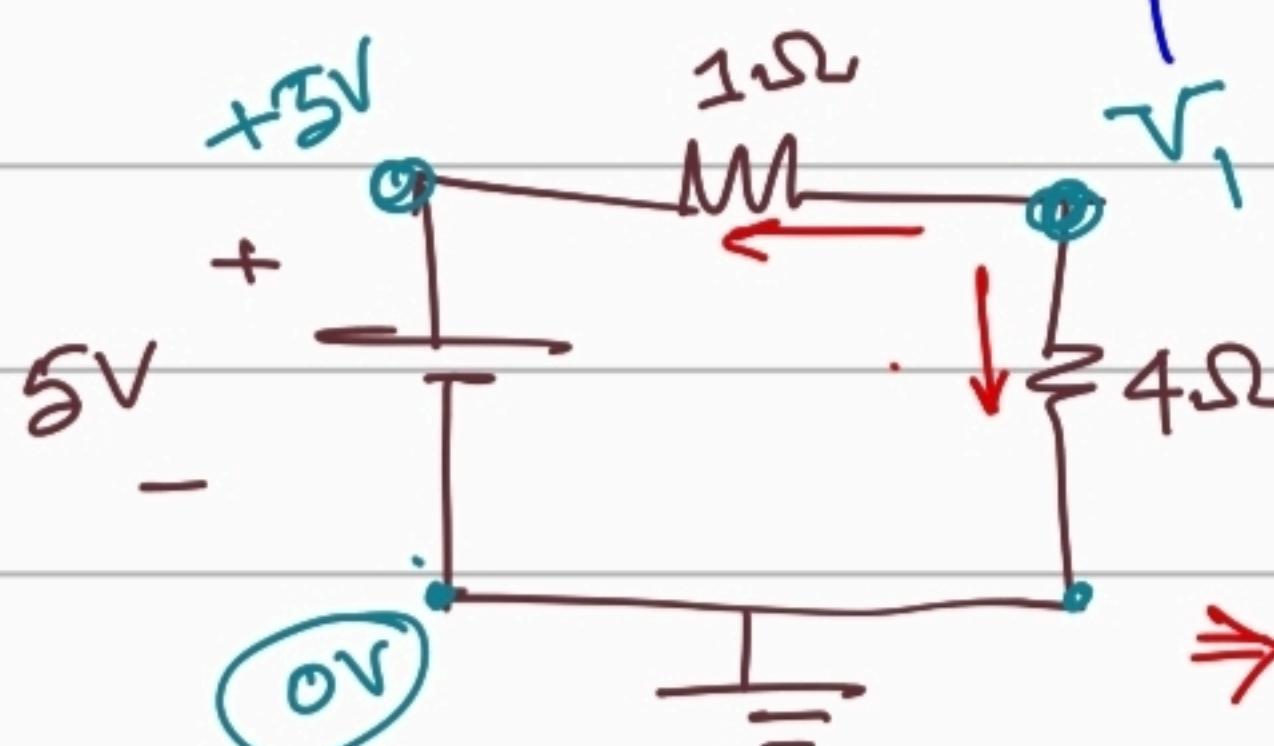



V_1 :

$$\frac{\text{V}_1 - 0}{4} + \frac{\text{V}_1 - 5}{1} = 0$$

$$\Rightarrow \text{V}_1 \left(\frac{1}{4} + 1 \right) = 5$$

$$\Rightarrow \text{V}_1 \cdot \frac{5}{4} = 5 \Rightarrow \text{V}_1 = 4\text{V}$$

Example : 2

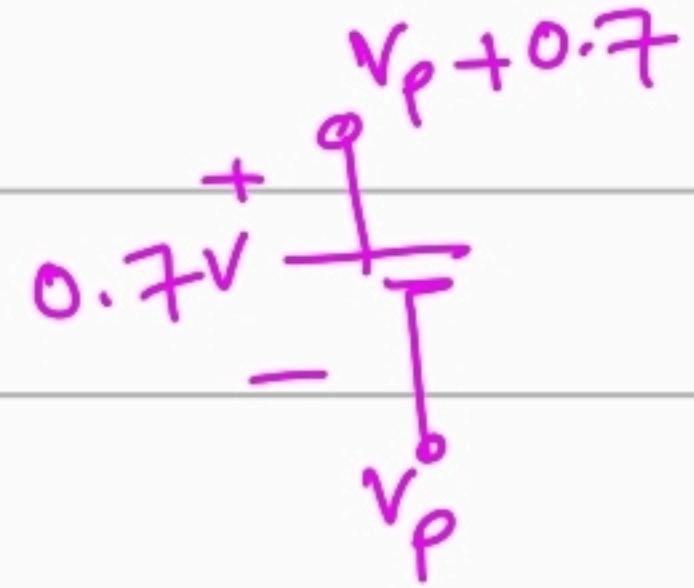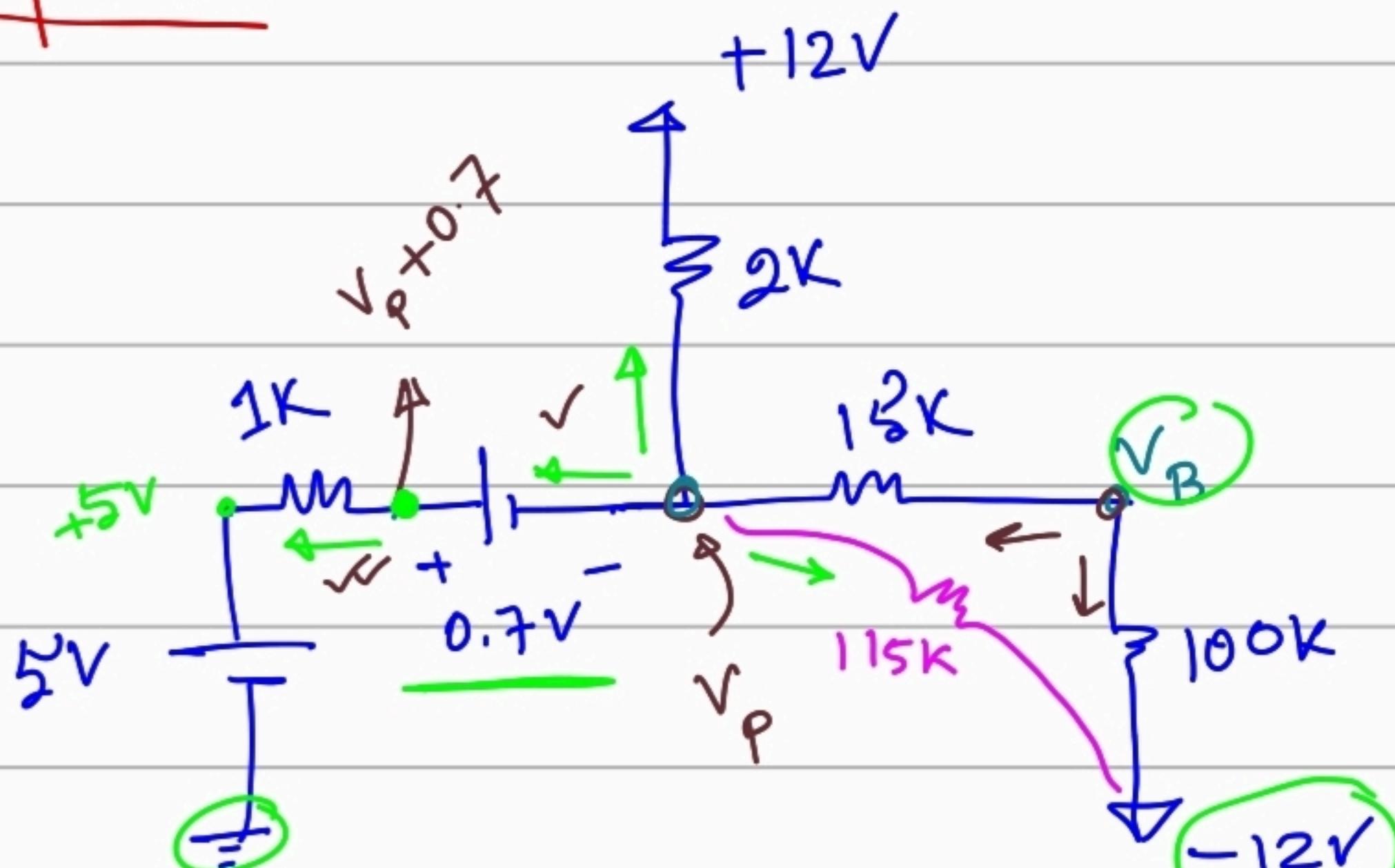

Online
Calculator

$$\text{(KCL)} \quad \frac{V_P - (-12)}{115} + \frac{V_P - 12}{2} + \frac{(V_P + 0.7) - 5}{1} = 0$$

$$V_P : \left. \begin{aligned} & \frac{V_P - V_B}{15K} + \frac{(V_P - 12)}{2} + \frac{(V_P + 0.7) - 5}{1} = 0 \\ & \frac{V_B - (-12)}{100} + \frac{(V_B - V_P)}{15} = 0 \end{aligned} \right\}$$

$$V_B : \frac{V_B - (-12)}{100} + \frac{(V_B - V_P)}{15} = 0$$

CSE 251 Review

Electronic Circuits and Devices.

Electronic : The method or process by which we can control the flow of electron using external forces / voltage.

Spintronics, Photonics, Twistrionics, Valleytronics
 Optoelectronics | roughly


Materials can be classified into three categories based on their conductivity.

1. Metal (Good conductor)



2. Semiconductors

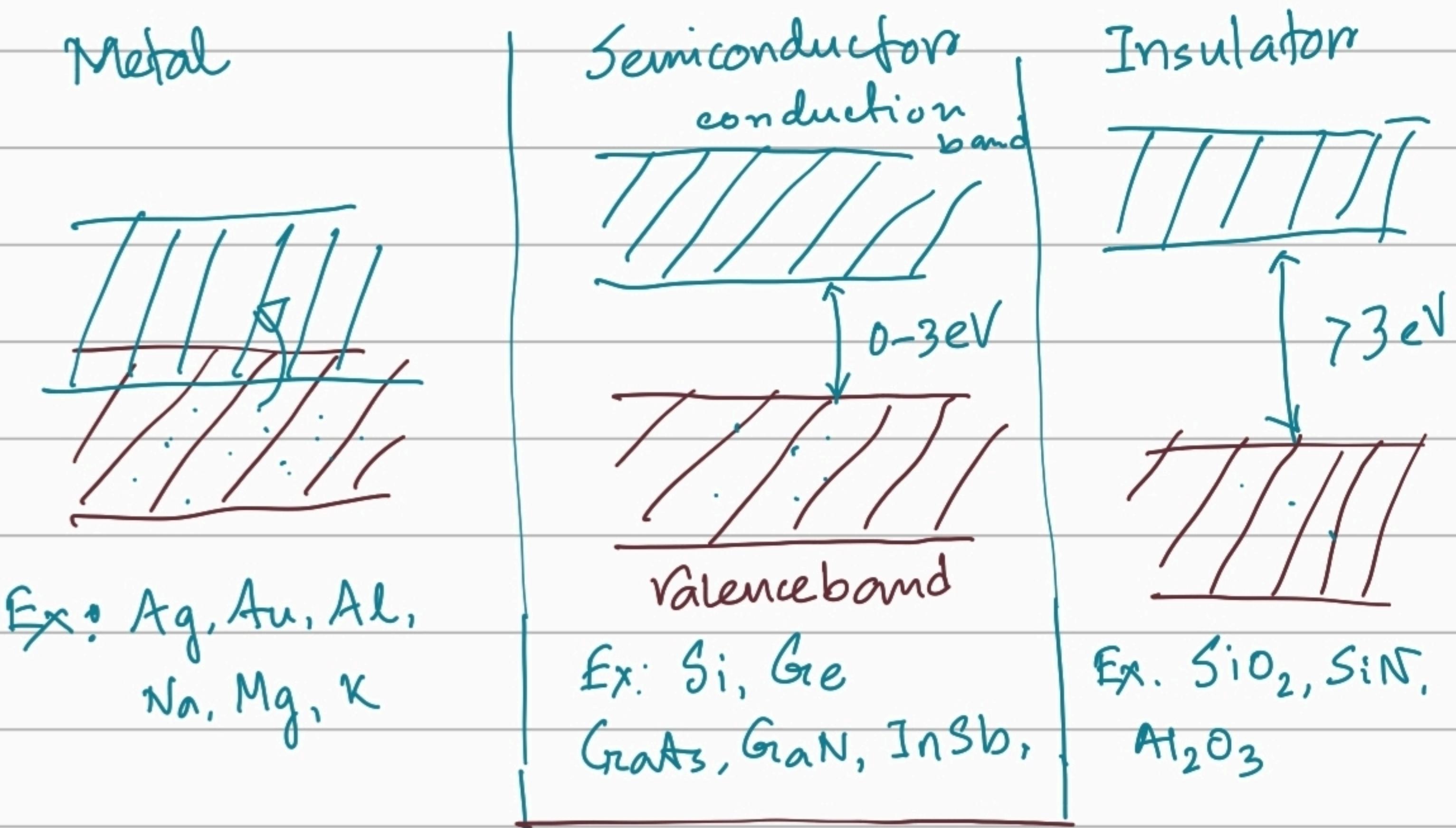3. Insulators (Bad conductor)

Electron's energy levels form energy bands within a solid. (Quantum Mechanics)



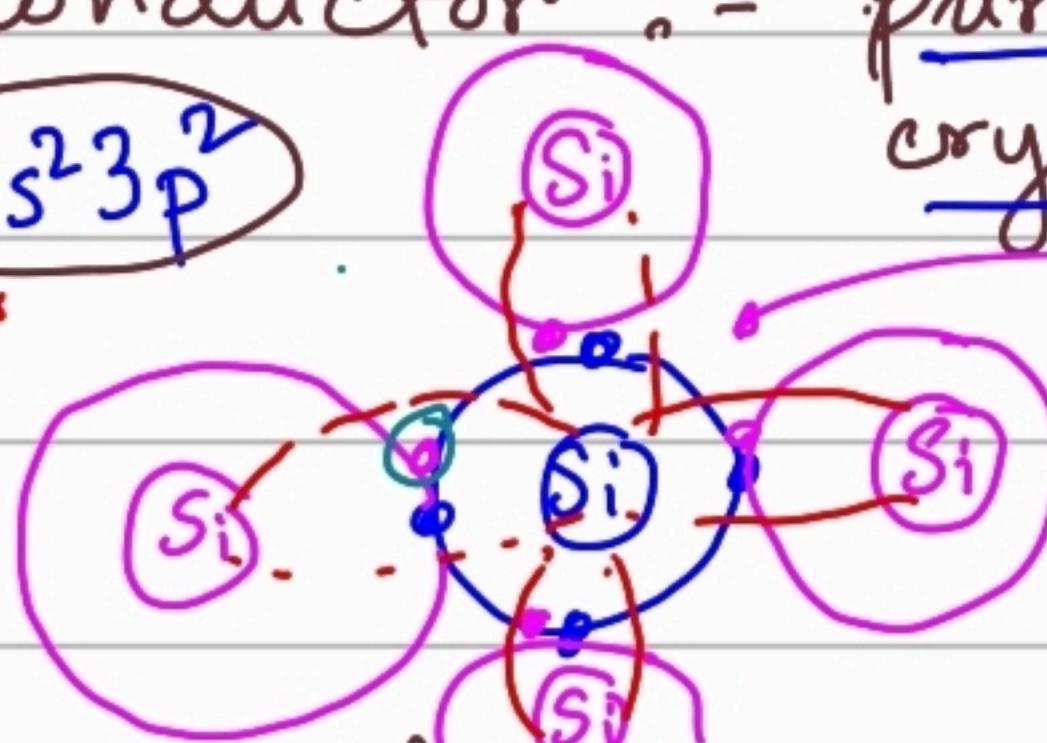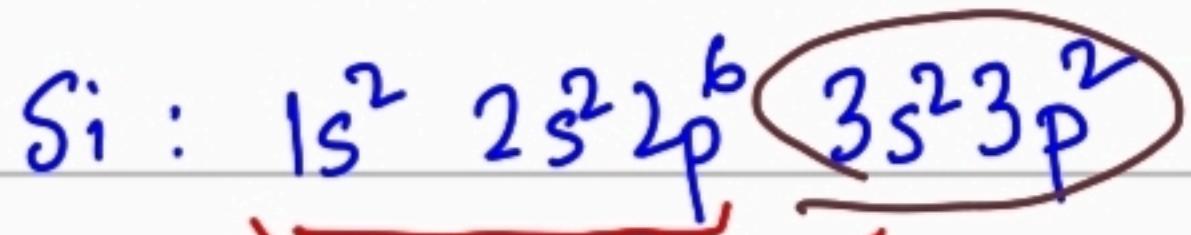Intrinsic Semiconductor :- pure semiconductor




crystal (Si)

covalent bond


Extrinsic Semiconductor :- impurities are introduced artificially.

① P-type semiconductor: Doping \rightarrow introduction of different atom in pure crystal.

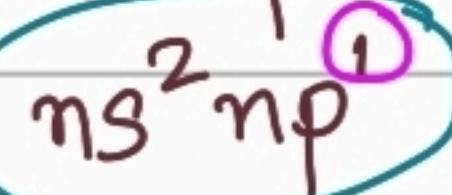Dopant atom : Group III A, Group 13 (B, Al)



$n = 2, 3, 4, \dots$

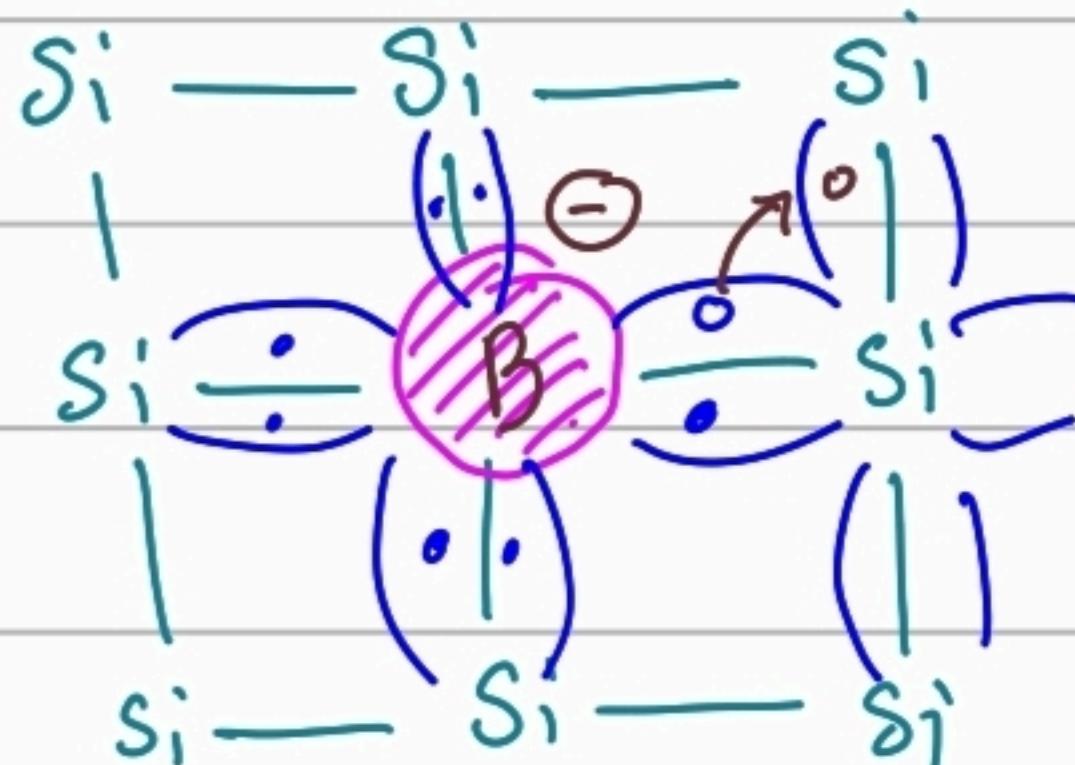


majority charge carrier is called hole. (h^+)

bound charge (-ve)

N-type Semiconductor :- Dopant atom : Group V, G-15



$ns^2 np^3$


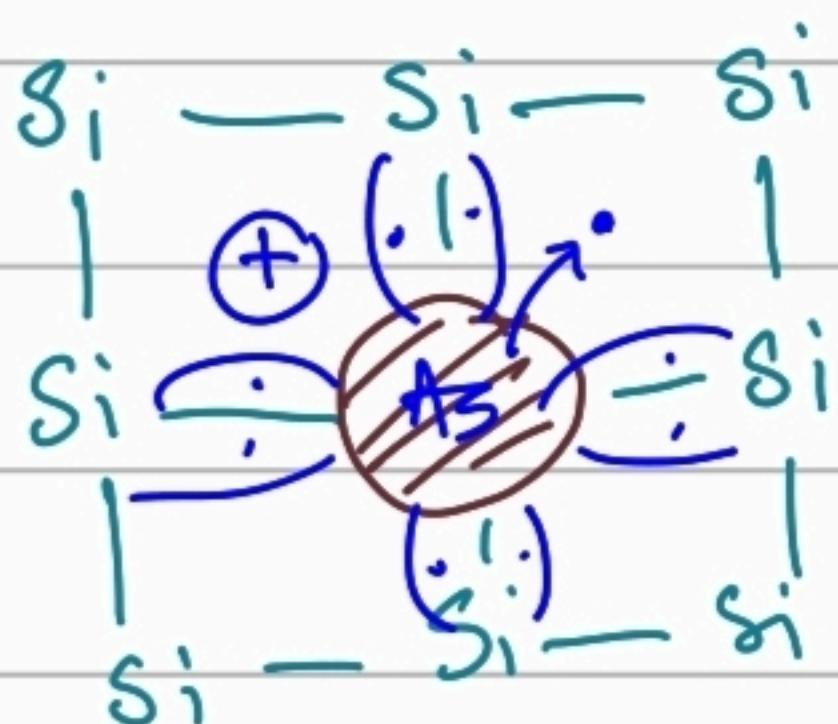


majority carrier \Rightarrow electron

bound charge is (-ve)

P-n junction diode :-

① Reverse Bias :-

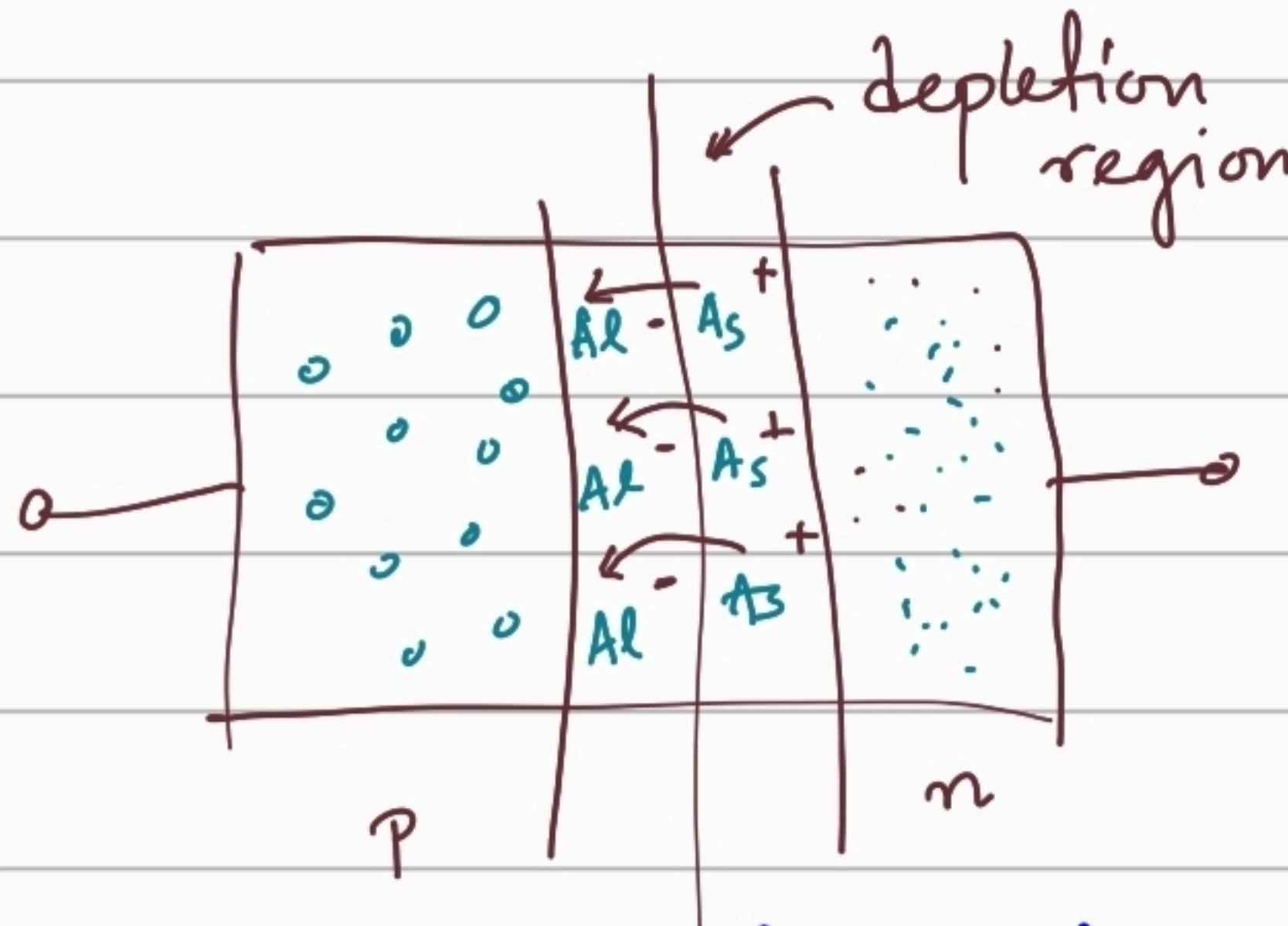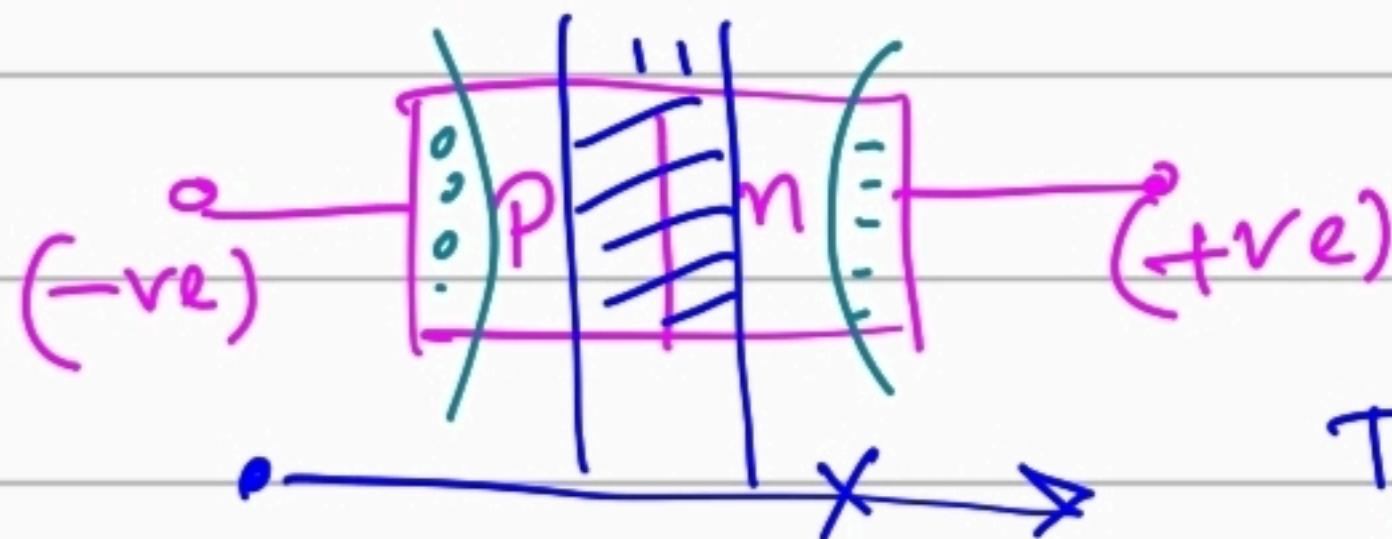


There is no current conduction in case of reverse bias.


Forward bias :-

$$Si, V_D > 0.6 \sim 0.7V$$

$$Ge, V_D 0.2 \sim 0.3V$$

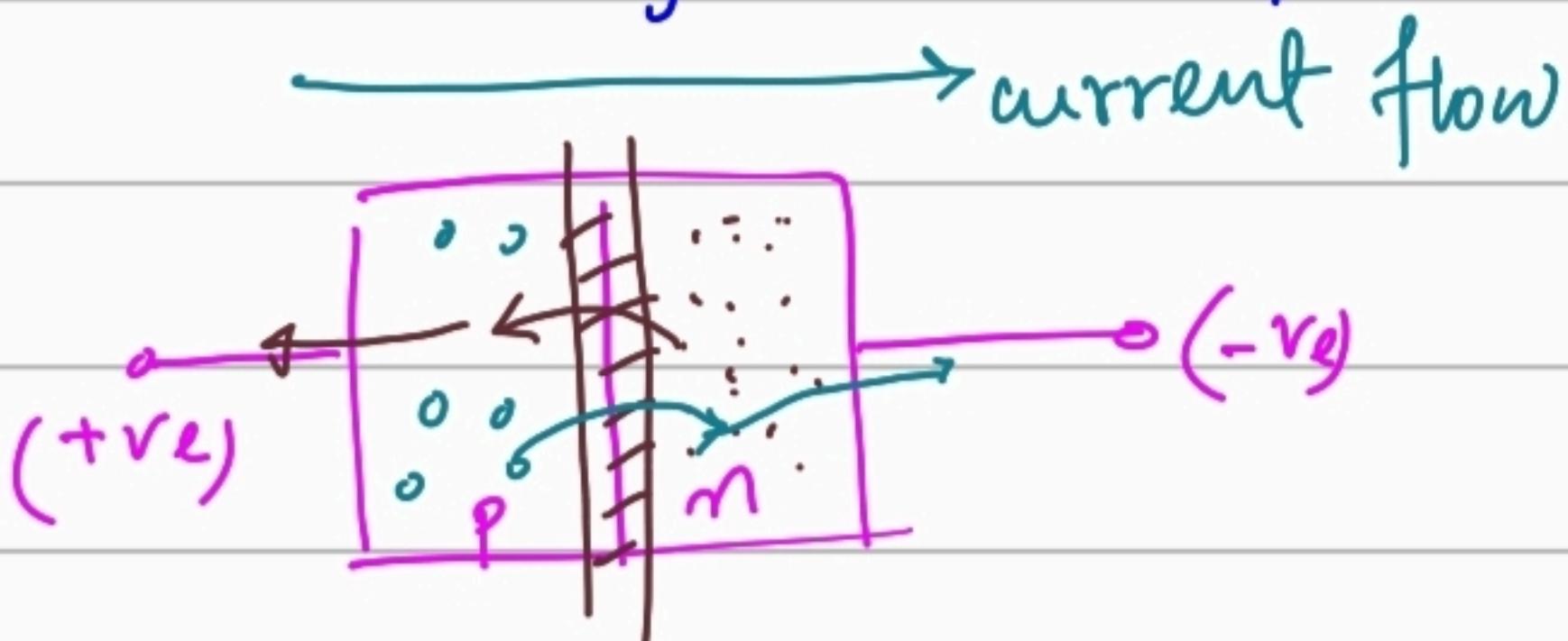

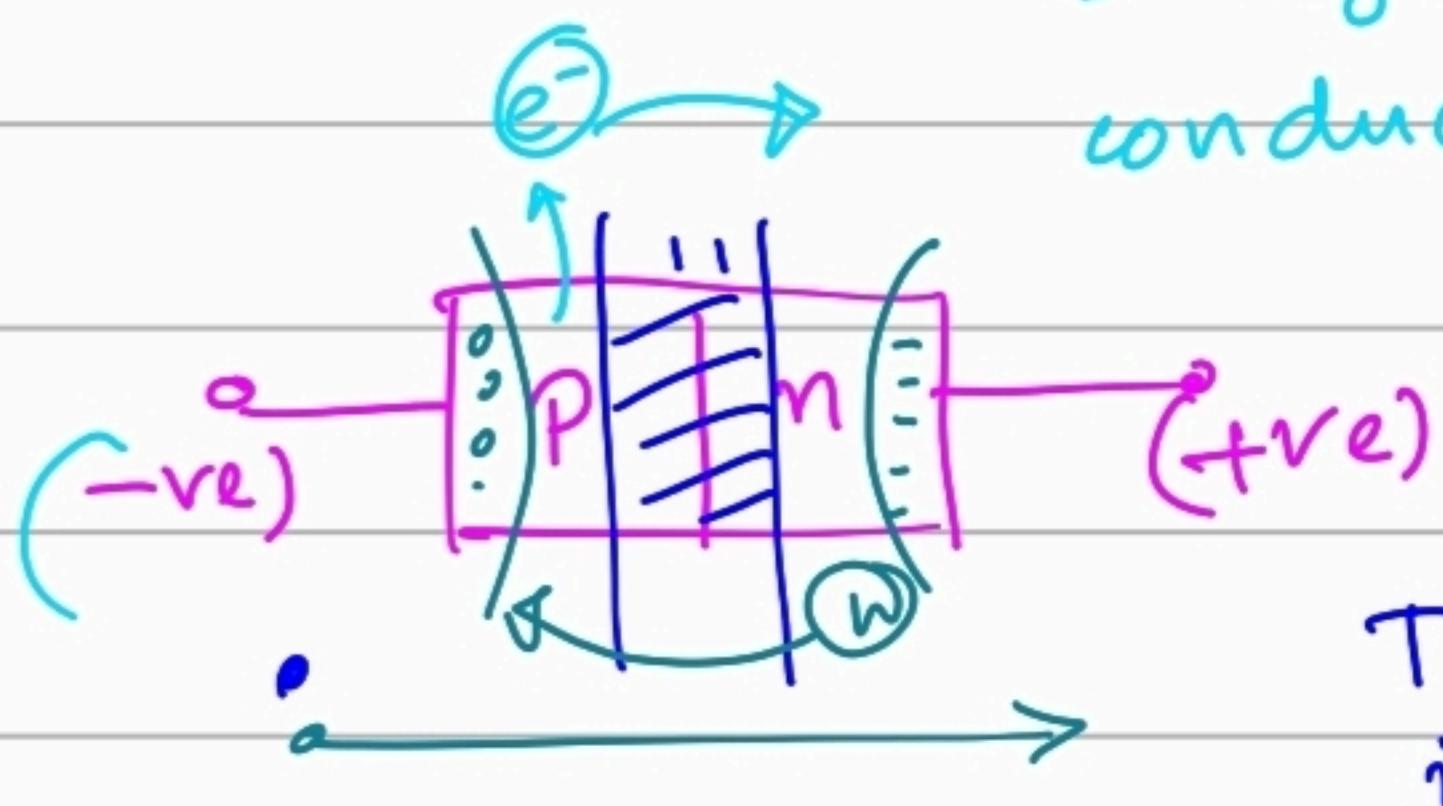Breakdown :- If the applied reverse bias voltage is high then diode might start conduction.



typical Si diode 25V

Zener diode $\sim 5\text{V}, 10\text{V}$

Diode \rightarrow constant voltage drop model


$$\textcircled{1} \quad \begin{array}{c} \xrightarrow{\hspace{1cm}} \\ \text{diode} \\ + 0.7\text{V} - \end{array} = \begin{array}{c} \xrightarrow{\hspace{1cm}} \\ \text{voltage source} \\ + 0.7\text{V} - \end{array}$$

Diode conduction voltage, $V_D = 0.7\text{V}$

$$\textcircled{2} \quad \begin{array}{c} \xrightarrow{\hspace{1cm}} \\ \text{diode} \\ - \cancel{+} + \end{array} = \begin{array}{c} \xrightarrow{\hspace{1cm}} \\ \text{open circuit} \end{array}$$

③ Activation / Threshold / Turn on voltage:

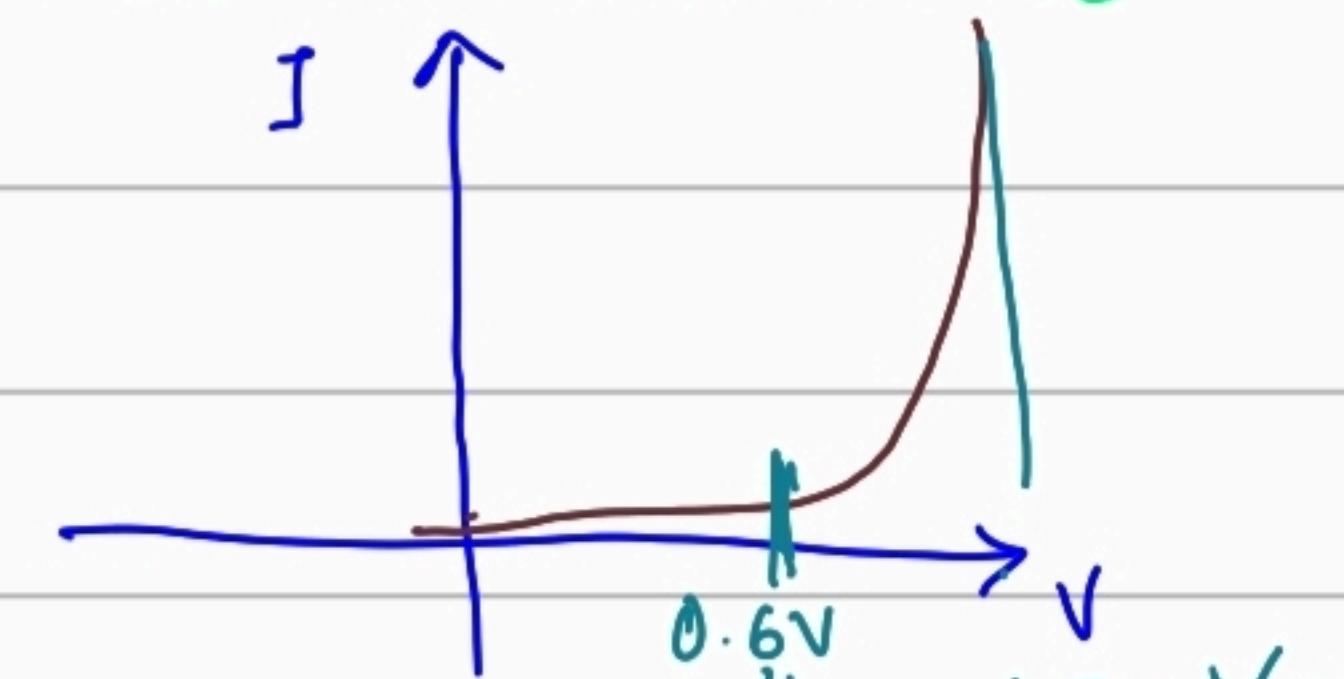The minimum voltage required to turn on a diode. $V_{th}(\text{diode}) = 0.6\text{V}$




④ Zener Diode:

$$\begin{array}{c} \xrightarrow{\hspace{1cm}} \\ \text{zener diode} \\ + \cancel{-} - \end{array} \quad V_D = 0.7\text{V} \quad \begin{array}{c} \xrightarrow{\hspace{1cm}} \\ \text{zener diode} \\ - \cancel{+} + \end{array} = \begin{array}{c} \xrightarrow{\hspace{1cm}} \\ \text{voltage source} \\ -V_{ZN} + \end{array}$$

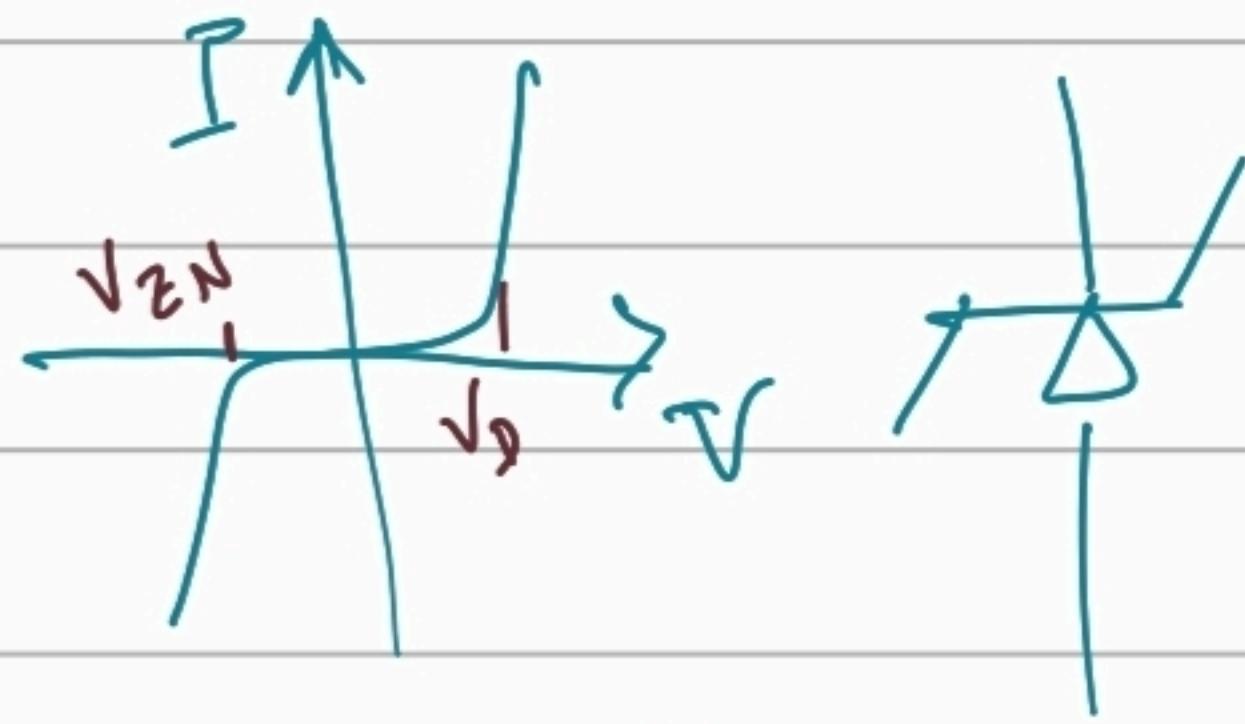0.6V $0.7 = V_D$

If the applied reverse bias voltage is higher than V_{ZN} , Zener diode starts conducting.





Transistor: Switching Device (Amplification)

n-p-n

Bipolar Junction Transistor (BJT)

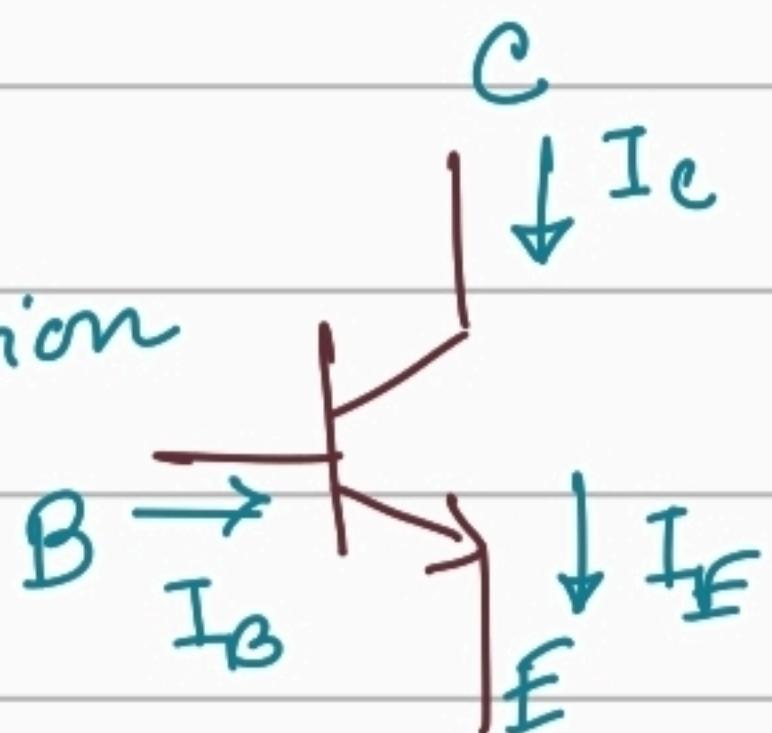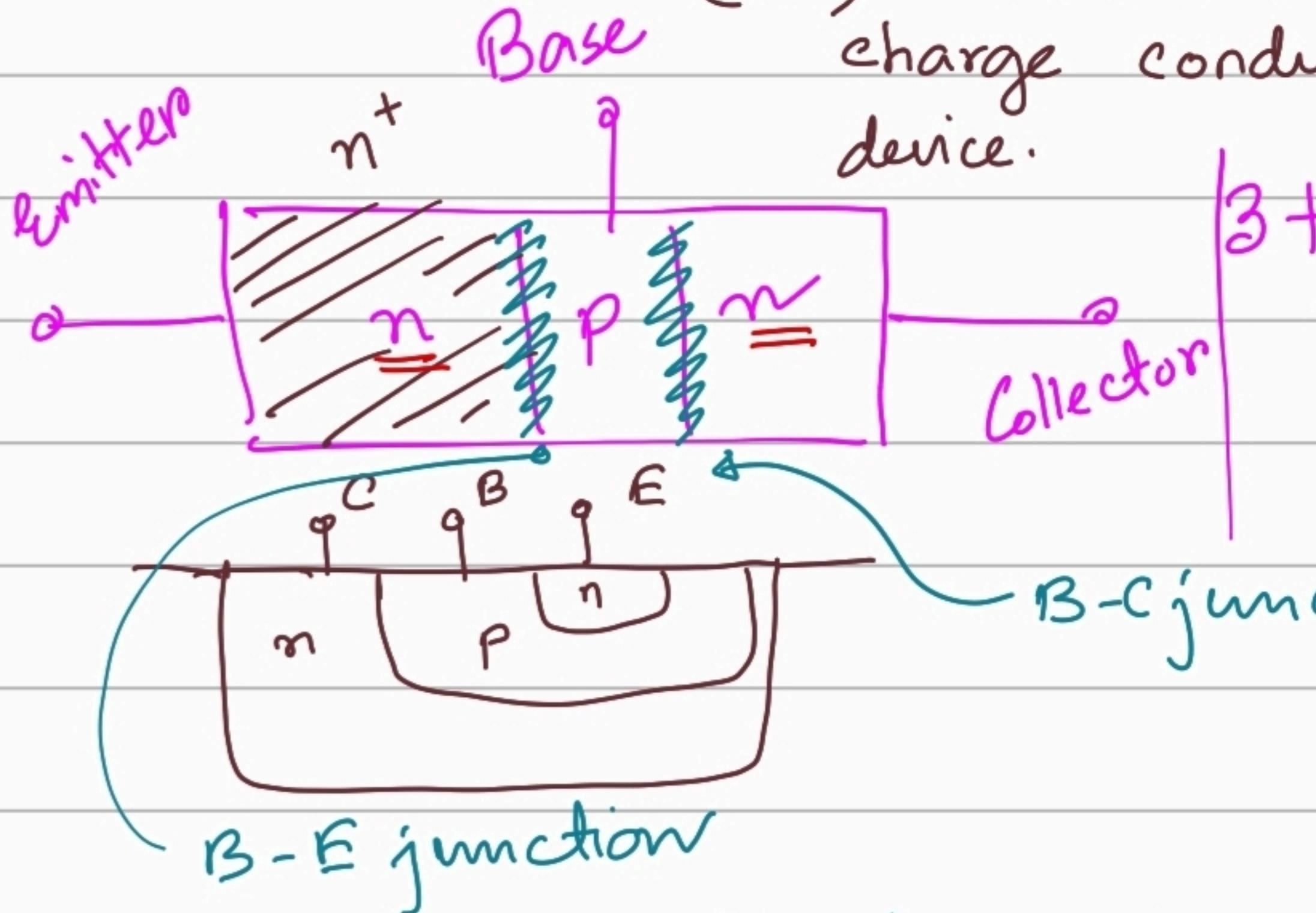(e-n) both are responsible for charge conduction in this device.



Depending junctions' operating mode BJT's operating mode can be classified into four different categories.

B-C junction	B-E junction	mode
Reverse	Forward	Forward Active (FA)
<u>forward</u>	<u>forward</u>	<u>Saturation (S)</u>
Reverse	Reverse	Cutoff (C)
<u>forward</u>	<u>reverse</u>	<u>Reverse Active (RA)</u>

Reverse Active:

Emitter and Collector switch their roles.

$$V_{BC} = 0.7V, \frac{I_E}{I_B} = \beta_R$$

reverse β

$$\beta_R \sim 0.1, 0.2, 0.3$$

$$V_C < V_B < V_E$$

Cutoff: ($V_{BE} \leq 0, V_{BC} \leq 0$)

$V_{BE} < V_\gamma$ (transistor)
= cut-in voltage / turn on voltage
 $= 0.5^2 V$

$$I_C = I_B = I_E = 0$$

V_{BC}

Saturation

$$V_{BE} > 0, V_{BC} > 0$$

$$V_{BE} = 0.8V$$

$$V_{CE} = 0.2V / 0.1V$$

$$V_{BC} = V_{BE} - V_{CE} = 0.6 / 0.7V$$

Checking condition:

$$\frac{I_C}{I_B} = \beta_{\text{forced}} < \beta_F (\text{Forward})$$

Forward Active

V_{BF}

$$V_{BE} > 0, V_{BC} < 0$$

$$30, 50, 100$$

$$V_{BE} = 0.7, \frac{I_C}{I_B} = \beta_F$$

Forward β , common emitter current gain

Checking condition:-

$$V_{CE} > 0.2V$$

$$I_C + I_B = I_E$$



: Introduction to Digital Logic Families

Digital logic design \rightarrow {



INVERTER



NAND



NOR

Digital logic family are different groups of electronic circuits that can be used to construct digital logic gates.