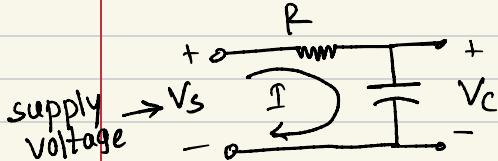


Signal Generators

→ Basic R-C Ckt:



- if $V_s > V_c \rightarrow$ capa store charge
- if $V_s < V_c \rightarrow$ capa discharge

for capacitor $\rightarrow [Q = CV]$

$$\hookrightarrow \text{Current, } I = \frac{dQ}{dt} = \frac{d(CV)}{dt} = C \frac{dV_c}{dt} \quad (\text{i})$$

$$\text{from ckt} \rightarrow I = \frac{V_s - V_c}{R} \quad (\text{ii})$$

equating (i) & (ii)

$$C \frac{dV_c}{dt} = \frac{V_s - V_c}{R} \quad (\text{iii})$$

We can determine the voltage across capacitor, $V_c(t)$ for the time $t_1 < t < \infty$ by solving the differential eqn (iii) -

$$\Rightarrow \int_{V_c(t_1)}^{\frac{dV_c}{dt}} \frac{dV_c}{V_s - V_c} = \frac{1}{R} dt \Rightarrow V_c(t) = V_s + (V_c(t_1) - V_s) \exp\left(-\frac{t-t_1}{RC}\right)$$



at $t \rightarrow \infty$ $V_c(\infty) = V_s \rightarrow V_{\text{final}}$

Time constant, $\tau = RC$

$$V_c(t) = V_{\text{final}} + (V_{\text{initial}} - V_{\text{final}}) \exp\left(-\frac{t-t_1}{\tau}\right)$$

Schmitt Oscillator / Astable Multivibrator:

↳ Square Wave generator.

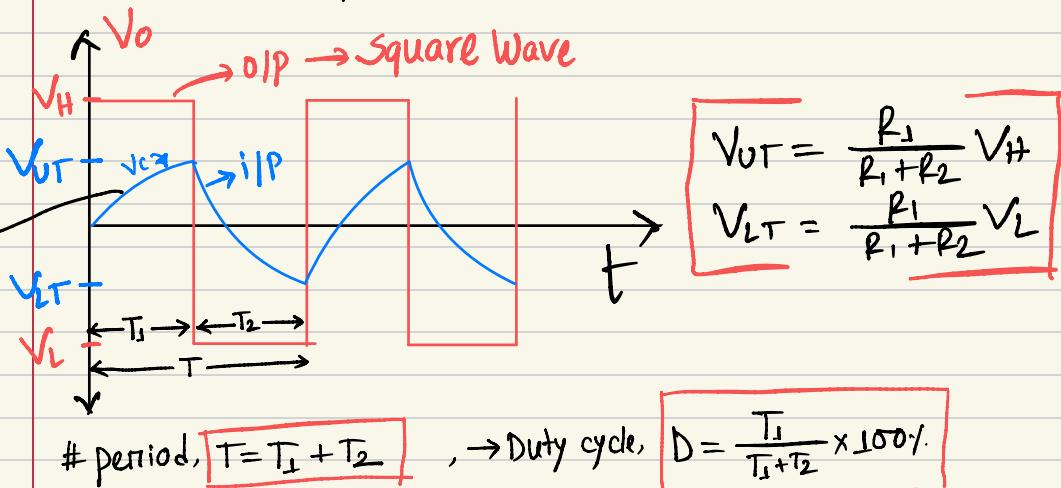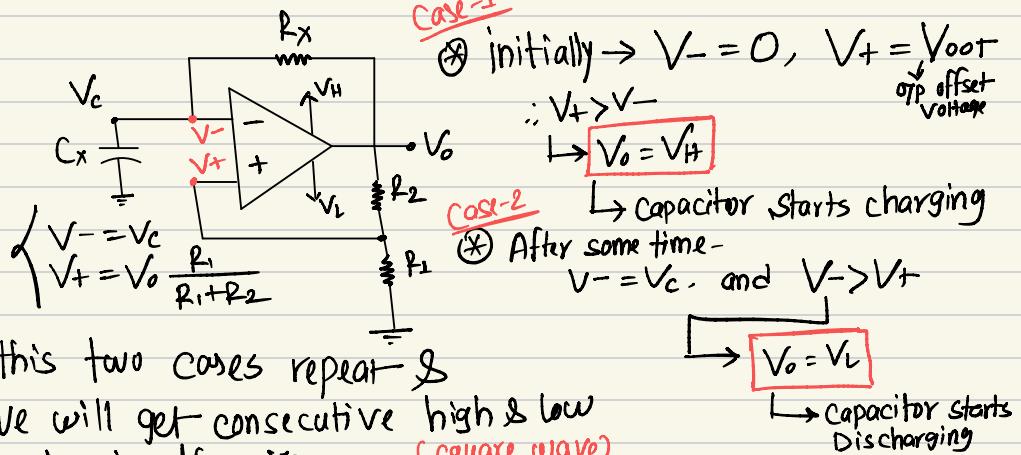

$$\rightarrow \text{Time const, } \tau = R_x C_x$$

$$\rightarrow V_c(t) = V_{\text{final}} + (V_{\text{initial}} - V_{\text{final}}) \exp\left(-\frac{t-t_1}{\tau}\right), V_{\text{final}} = V_o$$

$$\therefore t - t_1 = \tau \ln \left| \frac{V_o - V_c(t_1)}{V_o - V_c(t_2)} \right|$$

Case-1 :

$$0 < t < T_1$$

$$V_{\text{final}} = V_0 = V_H, \quad V_{\text{initial}} = V_{LT}$$

$$V_c(t) = V_H + (V_{LT} - V_H) \exp\left(-\frac{t-0}{R_x C_x}\right)$$

$$\text{at } t = T_1, \quad V_c(t) = V_{UT}$$

$$\therefore V_c(T_1) = V_{UT} = V_H + (V_{LT} - V_H) \exp\left(-\frac{T_1}{R_x C_x}\right)$$

$$\therefore T_1 = R_x C_x \ln \left| \frac{V_H - V_{LT}}{V_H - V_{UT}} \right|$$

Case-2 :

$$T_1 < t < T$$

$$V_{\text{final}} = V_0 = V_L, \quad V_{\text{initial}} = V_{UT}$$

$$\therefore V_c(t) = V_L + (V_{UT} - V_L) \exp\left(-\frac{t-T_1}{R_x C_x}\right)$$

$$\text{At } t = T \rightarrow V_c(t) = V_{LT}$$

$$\therefore V_c(t) = V_{LT} = V_L + (V_{UT} - V_L) \exp\left(-\frac{T-T_1}{R_x C_x}\right)$$

$$V_{LT} = V_L + (V_{UT} - V_L) \exp\left(-\frac{T_2}{R_x C_x}\right)$$

$$\therefore T_2 = R_x C_x \ln \left| \frac{V_L - V_{UT}}{V_L - V_{LT}} \right|$$

$$T = T_1 + T_2$$

Practice Problems

For the Schmitt trigger oscillator, the saturation output voltages are +10V and -5V. $R_1 = R_2 = 20\text{ k}\Omega$, $R_x = 50\text{ k}\Omega$ and $C_x = 0.01\text{ }\mu\text{F}$.

Determine the frequency and duty cycle.

→ Sol'n:

$$V_H = 10\text{ V}, V_L = -5\text{ V}$$

$$V_{UT} = \frac{R_1}{R_1 + R_2} V_H = \frac{20}{20+20} \times 10 = 5\text{ V}$$

$$V_{LT} = \frac{R_1}{R_1 + R_2} V_L = \frac{20}{20+20} (-5) = -2.5\text{ V}$$

$$\tau = R_x C_x = 50 \times 10^3 \times 0.01 \times 10^{-6} = 0.5 \times 10^{-3} \text{ s} \\ = 0.5 \text{ ms}$$

$$\rightarrow \text{now, } T_1 = \tau \ln \left| \frac{V_H - V_{LT}}{V_H - V_{UT}} \right| \\ = 0.5 \ln \left| \frac{10 - (-2.5)}{10 - 5} \right| = 0.458 \text{ ms}$$

$$\text{and, } T_2 = \tau \ln \left| \frac{V_L - V_{UT}}{V_L - V_{LT}} \right| = 0.5 \ln \left| \frac{-5 - 5}{-5 + 2.5} \right| \\ = 0.693 \text{ ms}$$

∴ Period, $T = T_1 + T_2 = 1.15 \text{ ms}$

∴ Frequency, $f = \frac{1}{T} = 0.868 \text{ kHz} = 868 \text{ Hz}$

∴ Duty cycle, $D = \frac{T_1}{T} \times 100\% = 39.82\%$

(Ans.)