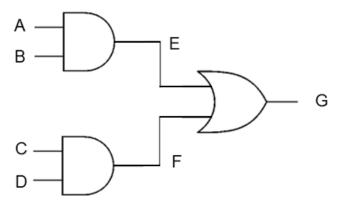




1. Design a CMOS logic circuit to implement the given compound gate in Figure below. First derive the logical expression of output Y and then design the CMOS network.



- 2. a) Design a static CMOS logic circuit that implements the logic function Y= AB
  - b) Design a static CMOS logic circuit that implements the logic function Y= (A+B)
- 3. Design a static CMOS logic circuit that will implement the following logic
  - a. NAND gate ( $Y = \overline{AB}$ )
  - b. XOR gate (  $Y = A\overline{B} + \overline{A}B$  )
- 3. Design a static CMOS logic circuit that will implement the following logic
  - a. NOR gate (  $Y = \overline{A + B}$  )
  - b. XNOR gate ( $Y = AB + \overline{AB}$ )
- 4. Design static CMOS circuit for the following expression,

a. 
$$Y = AB + CD$$

b. 
$$Y = AB + C$$

c. 
$$Y = (A+B)C$$

d. 
$$Y = (A+B)(C+D)$$

e. Y = 
$$\overline{AB + CD}$$

f. Y = 
$$\overline{AB + C}$$

g. 
$$Y = \overline{(A + B)C}$$

g. 
$$Y = \overline{(A + B)C}$$
  
h.  $Y = \overline{(A + B)(C + D)}$   
i.  $Y = \overline{A} + \overline{B} + \overline{C}$ 

i. 
$$Y = \overline{A} + \overline{B} + \overline{C}$$

5.

Truth Table


Input A	Input B	Output
0	0	1
0	1	0
1	0	0
1	1	1

Design a static CMOS logic circuit that will implement the above truth table.

CMOS logie design 1. AB + CD e Mos,






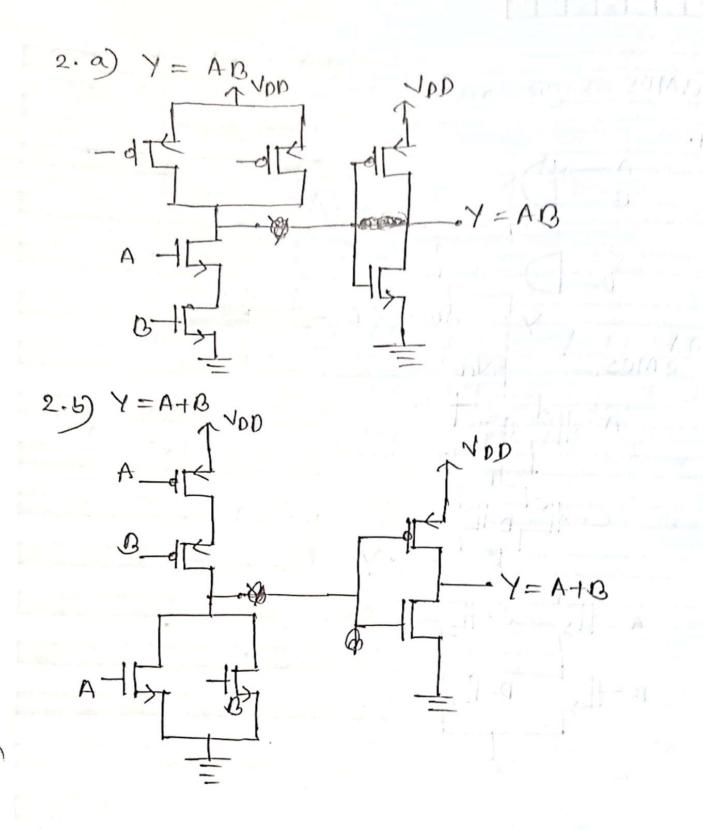







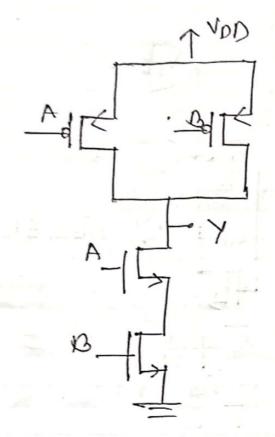








AB + AB TVDD VDD AT +AO = AB+AB



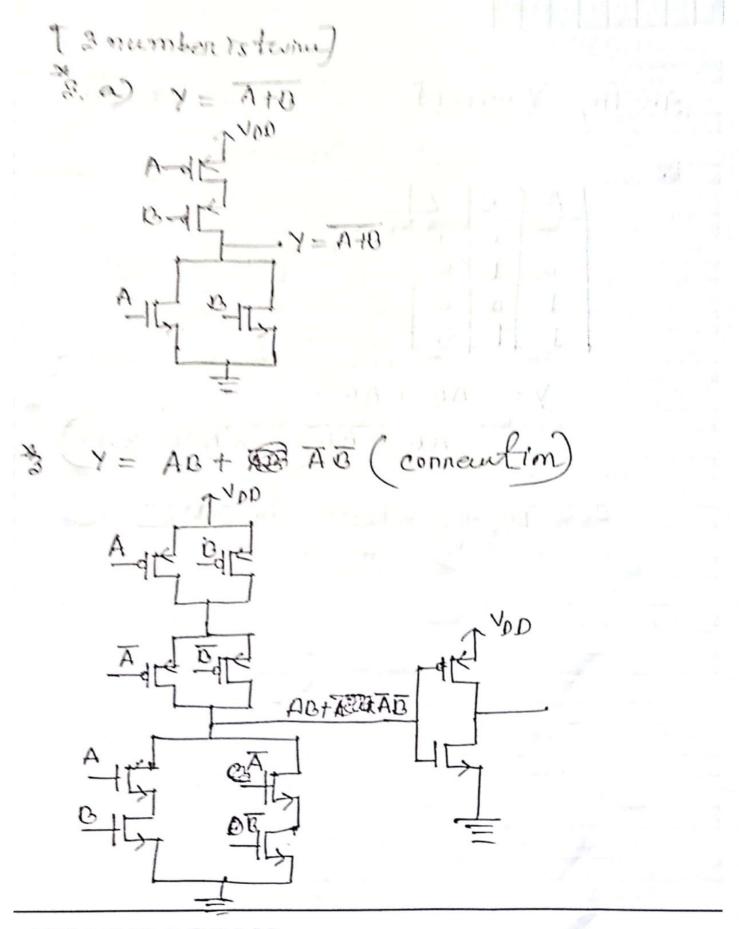web: www.ulkasemi.com e-mail: info@ulkasemi.com









## 4. Try Yourself

5.

A	Q	Y
0	0	1
0	1	0
1	0	0
1	1	0

$$Y = \overline{A0} + \overline{A0}$$
  
=  $A0 + \overline{A0}$  (XNOR Gale)

See previous solution for CMOS
(3(6))



web: www.ulkasemi.com e-mail: info@ulkasemi.com



60

8