

*8. Suppose you want to design a street light controller. You have a sensor that gives output as voltage as proportional to the light intensity. You need to switch off the light when the output of the sensor is above 5V. You need to switch on the light when the sensor output is below the 5V. (You can assume the V_H and V_L value)


- Draw the voltage transfer characteristic curve (V_{in} vs V_{out} plot). Clearly label the plot.
- Draw the circuit diagram that can be perfect for this specification.
- Find out the parameter value of the circuit.

9. Suppose you want to design a street light controller. You have a sensor that gives output as voltage as proportional to the light intensity. You need to switch off the light when the output of the sensor is above 5V. You need to switch on the light when the sensor output is below the 5V. There is a noise source of 1V peak-peak. Your instructor has told you to use a schmitt trigger circuit to improve performance. (You can assume the V_H and V_L value)

- What V_{TH} and V_{TL} value can be used for this design to solve the problem of noise?
- Draw the voltage transfer characteristics curve (V_{in} vs V_{out} plot) and clearly label the plot.
- Draw the circuit diagram that can be perfect for this specification.
- Find out the parameter value of the circuit.

Square Wave Generator

1.

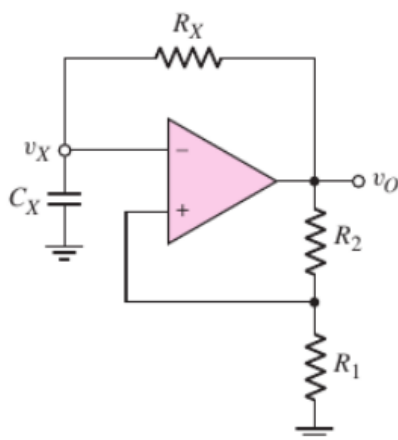


Here suppose $R_1 = 10k$, $R_2 = 20k$, $R_X = 1k$, $C_X = 1 \text{ mF}$, $V_H = 10V$ and $V_L = -10V$

- Find the period and frequency of the square wave?

- b. What will be the value of the duty cycle of the square wave?
- c. Draw the output waveform with proper labeling.


2.

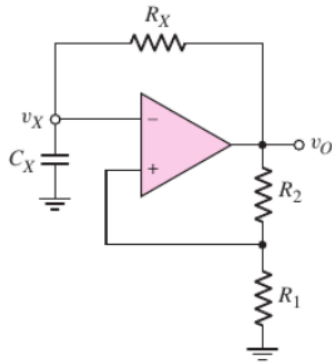

Here $V_H = 10\text{ V}$ and $V_L = -10\text{ V}$

Design the circuit so that it can generate a square wave with 1 kHz frequency and 50% duty cycle.


3.

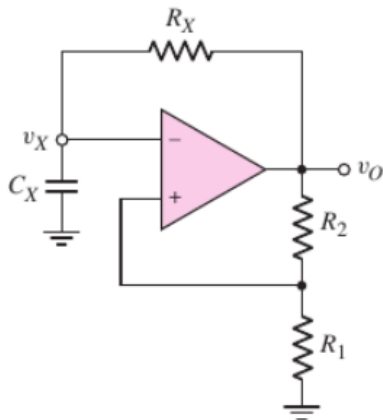

suppose $R_1 = 10\text{ k}$, $R_2 = 20\text{ k}$, $R_x = 1\text{ k}$, $C_x = 1\text{ mF}$

Design the circuit so that it can generate square wave with a 30% duty cycle. Find the frequency of your designed circuit.

4.

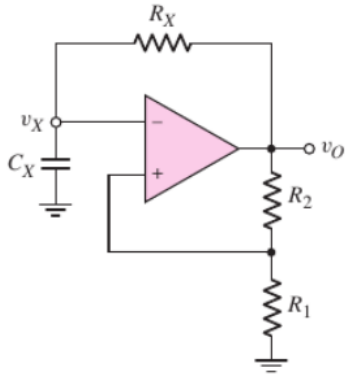


Here suppose $R_1 = 10k$, $R_2 = 20k$, $R_3 = 1k$, $C_X = 1 \text{ mF}$, $V_H = 10V$ and $V_L = -5V$

Find out the duty cycle of inverted output signal of the above circuit.


CMOS logic design

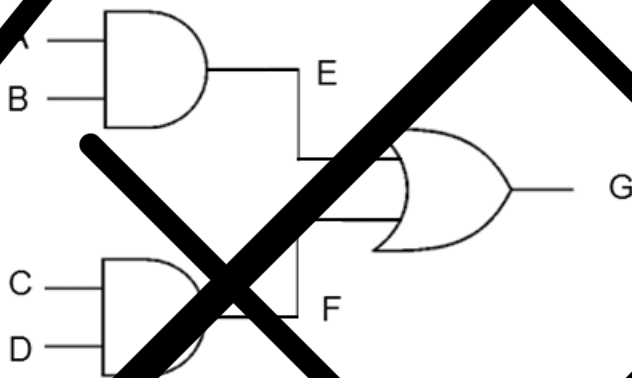1. Design a CMOS logic circuit to implement the given compound gate in Figure below. First derive the logical expression of output Y and then design the CMOS network.



2. a) Design a static CMOS logic circuit that implements the logic function $Y = AB$
b) Design a static CMOS logic circuit that implements the logic function $Y = (A+B)$
3. Design a static CMOS logic circuit that will implement the following logic
a. NAND gate ($Y = \overline{AB}$)
b. XOR gate ($Y = \overline{A}B + A\overline{B}$)
4. Design static CMOS circuit for the following expression,
a. $Y = AB + CD$

Square Wave Generation

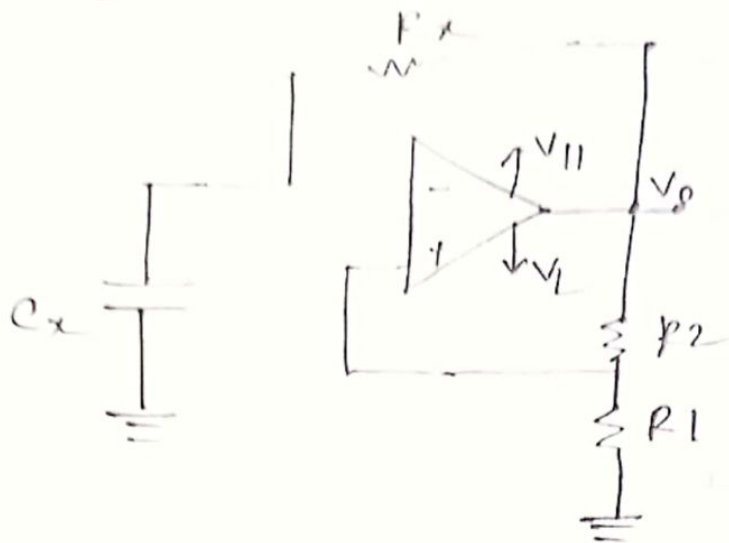

$$V_{TH} = V_H \frac{R_1}{R_1 + R_2}, \quad V_{TL} = V_L \frac{R_1}{R_1 + R_2}$$

$$T_1 = R_x C_x \ln \frac{V_H - V_{TL}}{V_H - V_{TH}}$$

$$T_2 = R_x C_x \ln \frac{V_L - V_{TH}}{V_L - V_{TL}}$$



ULKASEMI
We are Integrating your Ideas

web: www.ulkasemi.com
e-mail: info@ulkasemi.com

1. a) $R_1 = 10k, R_2 = 20k, R_x = 1k, C_x = 1mF,$

$$V_H = +10V, V_L = -10V$$

$$V_{TH} = \cancel{10V} V_H \times \frac{R_1}{R_1 + R_2}$$

$$= 10 \times \frac{10}{10 + 20} = 3.33$$

$$V_{TL} = V_L \times \frac{R_1}{R_1 + R_2} = -3.33$$

$$\tau = R_x C_x = 1k \times 1m = 1s$$

$$\begin{aligned} T_1 &= \tau \ln \frac{V_H - V_{TL}}{V_H - V_{TH}} \\ &= 1 \times \ln \frac{10 - (-3.33)}{10 - 3.33} \\ &= 0.69s \end{aligned}$$


$$\begin{aligned} T_2 &= \tau \ln \frac{V_L - V_{TH}}{V_L - V_{TL}} \\ &= 1 \times \ln \frac{-10 - 3.33}{-10 - (-3.33)} \\ &= 0.69s \end{aligned}$$

$$T = T_1 + T_2 = 0.69 + 0.69 = 1.38s$$

$$f = \frac{1}{T} = 0.72 \text{ Hz}$$

$$1. b) \text{ Duty cycle} = \frac{T_1}{T_1 + T_2} \times 100\%$$
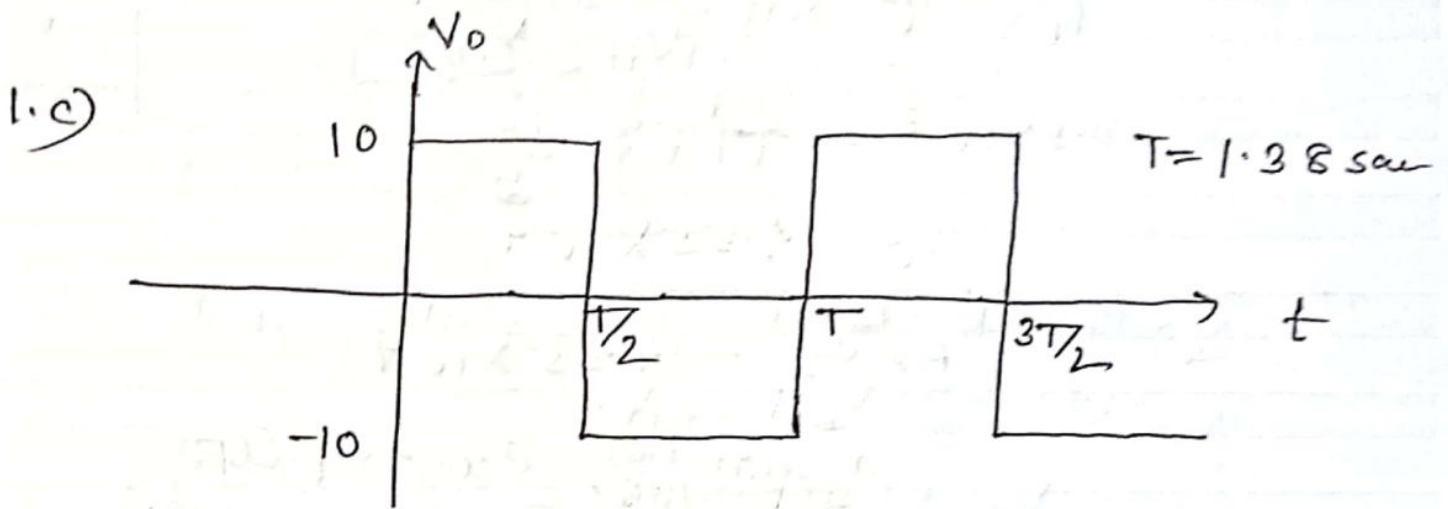
$$= \frac{0.69}{0.69 + 0.69} \times 100\% \\ = 50\%$$



$$2. \quad V_H = 10V, \quad V_L = -10V$$

Assuming, $R_1 = R_2 = 10k\Omega$

$$V_{TH} = V_H \times \frac{R_1}{R_1 + R_2} = 5V$$

$$V_{TL} = V_L \times \frac{R_1}{R_1 + R_2} = -5V$$

given, $f = 1kHz$, $T = \frac{1}{f} = 1ms$



ULKASEMI
We are Integrating your Ideas

web: www.ulkasemi.com
e-mail: info@ulkasemi.com

Duty cycle = 50% and, $T = T_1 + T_2$

$$\frac{T_1}{T_1 + T_2} = 0.5, \Rightarrow T_1 = T_2 = \frac{T}{2} = 0.5 \times 10^{-3}$$

$$T_1 = \tau \ln \frac{V_H - V_{TL}}{V_H - V_{TH}}$$

$$0.5 \times 10^{-3} = \tau \ln \frac{15}{5}$$

$$\tau = 4.55 \times 10^{-4}$$

$$R_x C_x = 4.55 \times 10^{-4}$$

assuming, $C_x = 1 \mu\text{F}$

$$R_x = \frac{4.55 \times 10^{-4}}{C_x} = 455 \Omega$$



ULKASEMI

We are Integrating your Ideas

web: www.ulkasemi.com
e-mail: info@ulkasemi.com

2. $\tau = R \times C = 1\mu \times 1mF = 1s$

$$\frac{t_1}{t_1 + t_2} = 0.3 = \frac{3}{10}$$

$$\frac{t_1}{t_2} = \frac{3}{7}$$

Assuming $R_1 = R_2 = 10$

$$t_1 = \tau \ln \frac{V_H - V_L}{V_H - V_{TH}}$$

$$t_1 = \tau \ln \frac{V_H - V_L \frac{R_1}{R_1 + R_2}}{V_H - V_H \frac{R_1}{R_1 + R_2}}$$

$$t_1 = \tau \ln \frac{V_H - V_L/2}{V_H - V_H/2}$$

$$t_1 = \tau \ln \frac{2V_H - V_L}{V_H}$$

$$t_2 = \tau \ln \frac{V_L - V_{TH}}{V_L - V_{TL}}$$

$$= \tau \ln \frac{V_L - V_H/2}{V_L}$$

$$t_2 = \tau \ln \frac{2V_L - V_H}{V_L}$$



ULKASEMI

We are Integrating your Ideas

web: www.ulkasemi.com
e-mail: info@ulkasemi.com

Now, $7T_1 = 3T_2$

$$\Rightarrow 7 \ln \frac{2V_H - V_L}{V_H} = 3 \ln \frac{2V_L - V_H}{V_L}$$

suppose, $V_H = 10V$,

Find $V_L = ?$ — 2.24 (use calculator)
solve eqn

4. $\tau = R \times C = 1s$

$V_H = +10V$, $V_L = -5V$

$$V_{TH} = V_H \frac{R_1}{R_1 + R_2} = 10 \times \frac{10}{10 + 20} = 3.33$$

$$V_{TL} = V_L \frac{R_1}{R_1 + R_2} = -5 \times \frac{10}{10 + 20} = -1.67$$

$$T_1 = \tau \ln \frac{V_H - V_{TL}}{V_H - V_{TH}} = 1 \times \ln \frac{10 - (-1.67)}{10 - 3.33} = 0.559$$

$$T_2 = \tau \ln \frac{V_L - V_{TH}}{V_L - V_{TL}} = 1 \times \ln \frac{-5 - 3.33}{-5 - (-1.67)} = 0.913s$$

Duty cycle = $\frac{T_1}{T_1 + T_2} \times 100\% = 37.9\%$