

③ & ④ can be used to change the transition voltage by tuning R_1 and R_2 . They are building block of schmitt trigger.

Schmitt Trigger:

→ Comparator with hysteresis




→ has two threshold voltages (References)

→ V_{UT} → upper threshold voltage.
→ V_{LT} → lower " "

Non-Inverting Schmitt trigger:


→ V_{UT} → low to high transition.

→ V_{LT} → high to low transition.

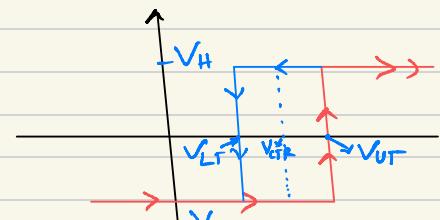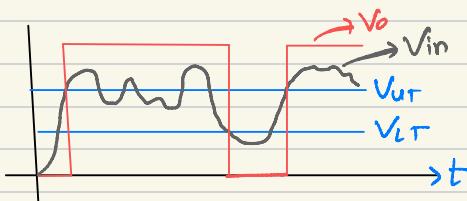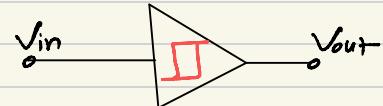

Transfer char. of Non. Inv. S.T.

Non. Inv. S.T. Ckt

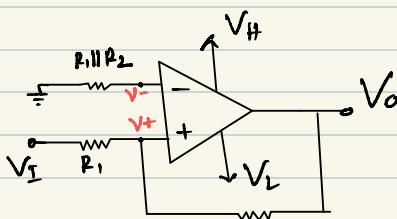


when $V_+ < V_- \rightarrow V_o = V_L$

$$; V_+ = V_L \frac{R_1}{R_1 + R_2} + V_f \frac{R_2}{R_1 + R_2} < 0$$

$$\therefore V_f < \left(-\frac{R_1}{R_2} \right) V_L$$

$$\therefore V_o = V_L$$
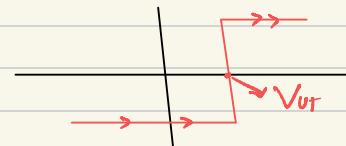
$$\therefore V_{fL} = -\frac{R_1}{R_2} V_L$$



$$\begin{cases} V_- = 0 \\ V_+ = V_o \frac{R_1}{R_1 + R_2} + V_f \frac{R_2}{R_1 + R_2} \end{cases}$$

When $V_+ > V_- \rightarrow V_o = V_H$


$$\therefore V_- = 0$$

$$V_+ = V_H \frac{R_1}{R_1 + R_2} + V_I \frac{R_2}{R_1 + R_2}$$


$V_+ > V_-$

$$\Rightarrow V_I > \left(-\frac{R_1}{R_2}\right) V_H \rightarrow V_o = V_H$$


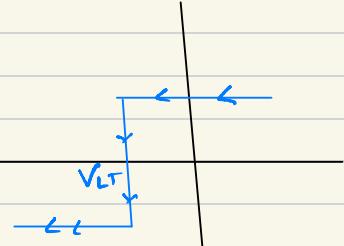
$$\therefore V_{LT} = \left(-\frac{R_1}{R_2}\right) V_H \quad \text{X}$$



Combined characteristics

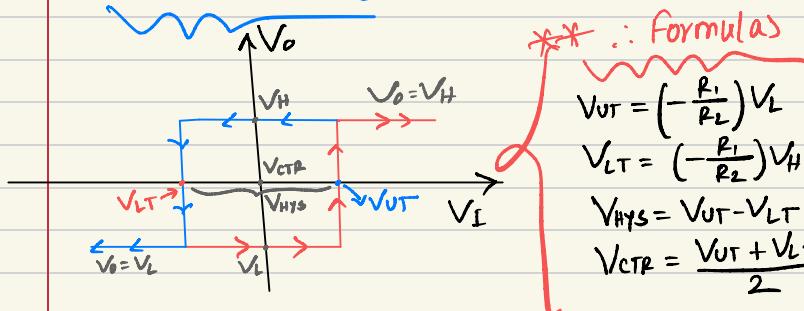

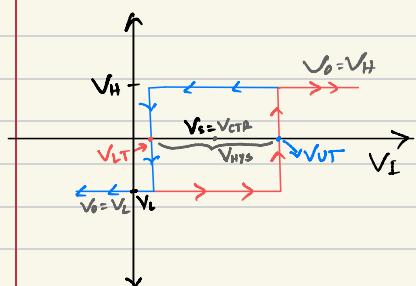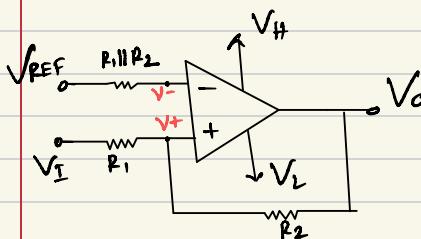Non-Inv. S.T. with applied voltage. (V_{REF})



**

$$V_- = V_{REF}$$

$$V_+ = V_o \frac{R_1}{R_1 + R_2} + V_I \frac{R_2}{R_1 + R_2}$$

$$V_{UT} = \left(-\frac{R_1}{R_2}\right) V_L + \left(\frac{R_1 + R_2}{R_2}\right) V_{REF}$$

$$V_{LT} = \left(-\frac{R_1}{R_2}\right) V_H + \left(\frac{R_1 + R_2}{R_2}\right) V_{REF}$$

$$V_{HYS} = V_{UT} - V_{LT}$$




$$V_{CTR} = \frac{V_{UT} + V_{LT}}{2} = V_S$$

shift voltage, V_S

$$V_S = \frac{R_1 + R_2}{R_2} V_{REF}$$


Inverting Schmitt trigger:

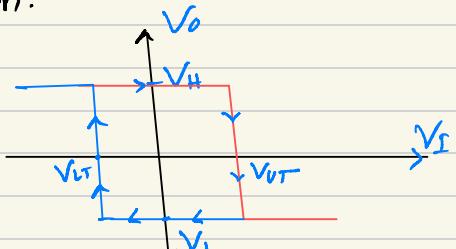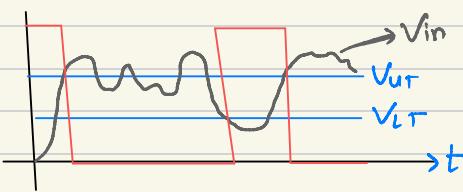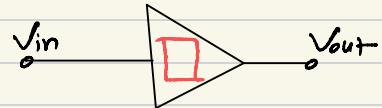- $V_{UR} \rightarrow$ high to low transition.
- $V_{LT} \rightarrow$ low to high transition.



Transfer char. of Inv S.T.

① Inv. S.T. Ckt

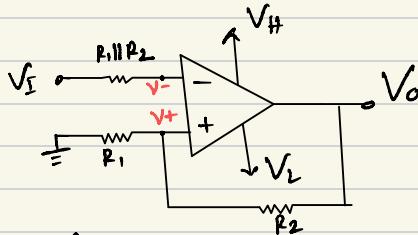

$$V_- = V_I$$

$$V_+ = V_o \frac{R_1}{R_1 + R_2}$$


When $V_- > V_+ \rightarrow V_o = V_L$

$$V_- = V_I$$

$$V_+ = V_L \frac{R_1}{R_1 + R_2}$$

$$V_- > V_+$$
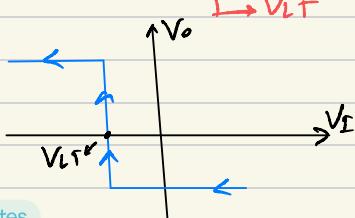
$$V_I > V_L \frac{R_1}{R_1 + R_2} \rightarrow V_o = V_L$$




when $V_- < V_+ \rightarrow V_o = V_H$

$$V_- = V_I$$


$$V_+ = V_H \frac{R_1}{R_1 + R_2}$$

$$V_- < V_+$$
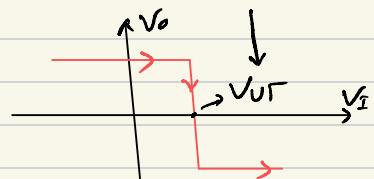
$$V_I < V_H \frac{R_1}{R_1 + R_2} \rightarrow V_o = V_H$$



combined char.

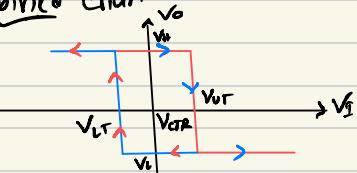

**Formulas



$$V_{UR} = V_H \frac{R_1}{R_1 + R_2}$$

$$V_{LT} = V_L \frac{R_1}{R_1 + R_2}$$

$$V_{HYS} = V_{UR} - V_{LT}$$

$$V_{CTR} = \frac{V_{UR} + V_{LT}}{2}$$

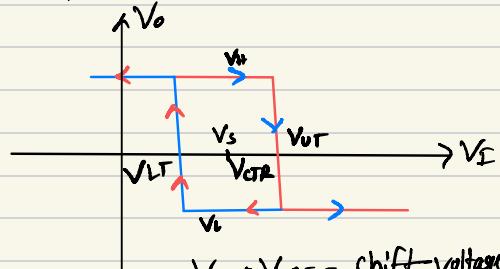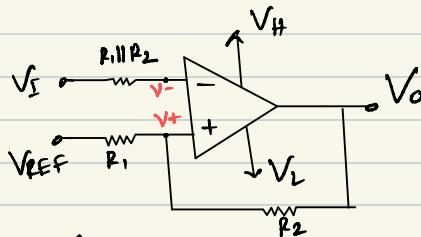(*) Inv. S.T. CKT with applied voltage (V_{REF})



$$V_- = V_I$$

$$V_+ = V_O \frac{R_1}{R_1 + R_2} + V_{REF} \frac{R_2}{R_1 + R_2}$$

$V_S \rightarrow V_{REF}$ = Shift voltage.

** Formulas

$$V_{UT} = V_H \frac{R_1}{R_1 + R_2} + V_{REF} \frac{R_2}{R_1 + R_2}$$

$$V_{LT} = V_L \frac{R_1}{R_1 + R_2} + V_{REF} \frac{R_2}{R_1 + R_2}$$

$$V_{HYS} = V_{UT} - V_{LT}$$

$$V_S = V_{CR} = \frac{V_{UT} + V_{LT}}{2} = V_{REF} \frac{R_2}{R_1 + R_2}$$

Practice problem

$$R_1 = 10\text{k}\Omega, R_2 = 90\text{k}\Omega, V_H = 10\text{V}, V_L = -10\text{V}$$

- Determine the followings for non-inverting Schmitt trigger.
→ $V_{UT}, V_{LT}, V_{HYS}, V_{CR}$

- Determine the values for inverting Schmitt trigger.

(*) Schmitt Trigger → Bistable multivibrator

because it has two stable states → $V_o = V_H \& V_L$

Application

- Smoke Detector
- Street Light Control

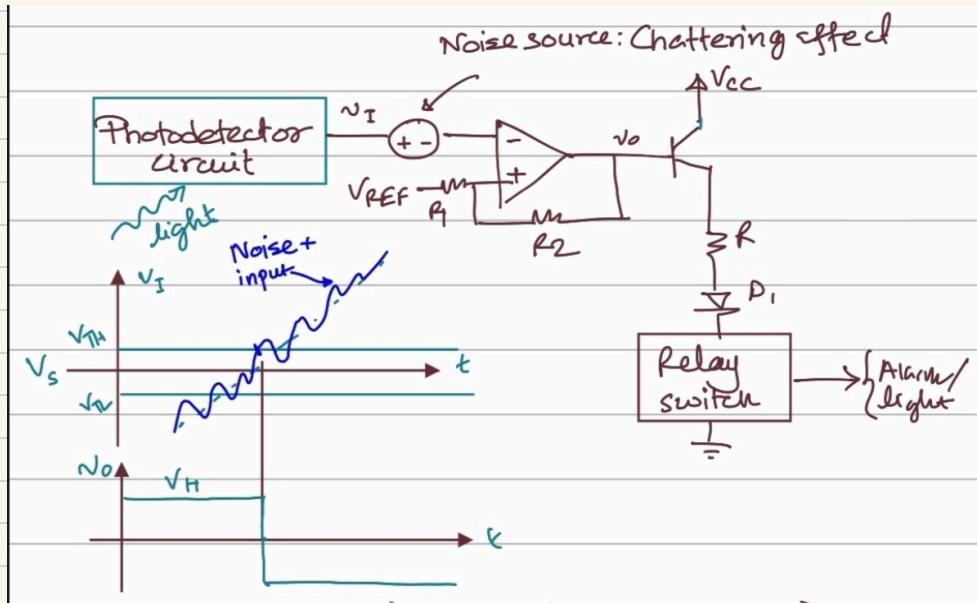


fig: Smoke Detector CKT

* Naemen → Design problem 15.7 → (final Exam)